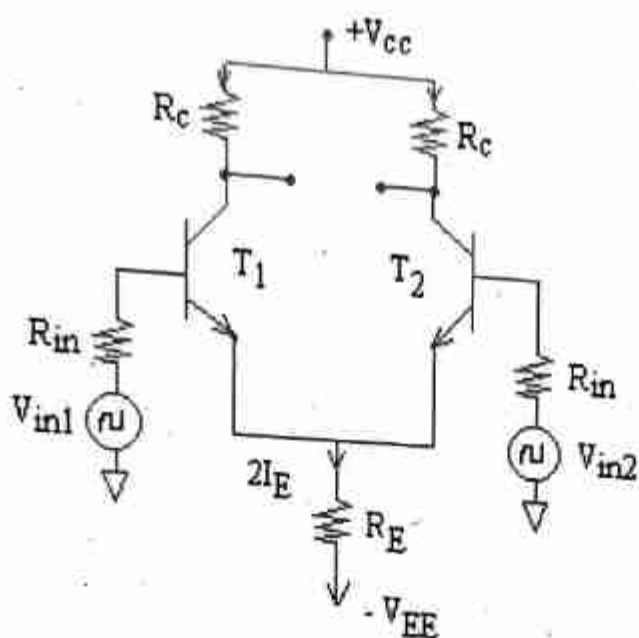


11. Operational Amplifier

DIFFERENTIAL AMPLIFIER

The differential amplifier is the most widely used circuit building block in analog integrated circuits. Differential amplifier is also a basis for high speed logic family (ECL). It also has applications in many other areas.

Differential amplifier consists of two identical emitter coupled transistors as shown below :



Differential amplifier amplifies the difference of two input signals $V_0 = A(V_{in1} - V_{in2})$

Configurations of Differential Amplifier

Differential amplifier can work in four different configurations :

- Dual Input balance output
- Dual input unbalance output
- Single input balance output
- Single input unbalance output.

Types of differential amplifier

Differential amplifier can work in two modes :

- Differential mode** : When two different inputs are applied at input terminals.
- Common mode** : When same input is applied to both the input terminals.

R_{in} = input impedance

$R_C = R_{C1} = R_{C2}$ with $R_E \gg r_e$

Common Mode :

When common input is applied at both input terminal which is given by $V_{CM} = \frac{V_{in1} + V_{in2}}{2}$


Common mode gain is given by $A_{CM} = \frac{V_0}{V_{CM}} = \frac{R_C}{2R_E}$

Ideally A_{CM} should be zero to avoid noise amplification. In order to achieve $A_{CM} = 0$ and R_E be infinity, different arrangement are made which we will see later.

Swamping Resistor :

As we know that differential gain of the differential amplifier depends on r_e . r_e itself is a temperature dependent which makes A_d temperature dependent in order to avoid this temperature dependence improves the linearity range ω_c incorporate R'_E (called swamping resistor) in series with emitter of transistor.

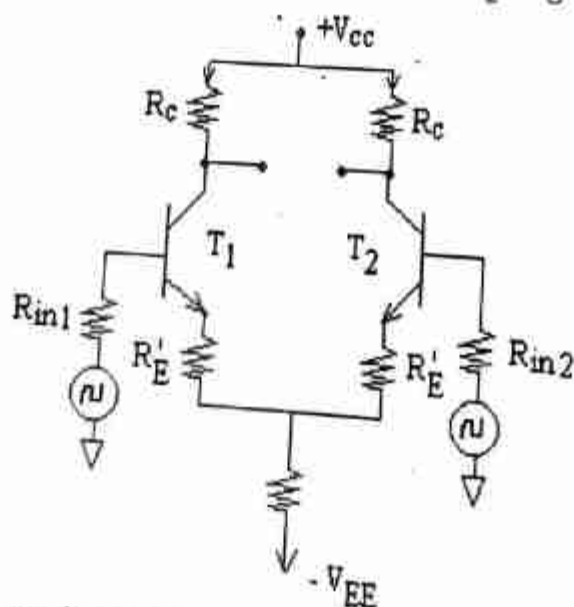R'_E should be large enough to swamp out the effect of r_e on gain.



Dual input balanced output configuration with swamping resistor.

Differential gain with R'_E

$$A_d = \frac{R_C}{r_e + R'_E}$$

If $R_E \gg r_e$ then $A_d = \frac{R_C}{R_E}$

i.e. A_d is independent of temperature variation.

$$R_m = 2\beta_{ac}(r_e + R_E)$$

$$R_{o1} = R_C; R_{o2} = R_C$$

Similarly the A_d and R_{in} at all other configuration can be achieved by replacing r_e by $(r_e + R_E)$.

Advantages :


Swamping resistor removes the temperature dependance of A_d (i.e. provides better stability). But A_d will decrease.

Addition of swamping resistor also increases the range of linearity.

Question 1: With following specification for the dual input balance output differential amplifier $R_C = 5k$, $R_{in1} = R_{in2} = 100\Omega$, $V_{CC} = 10V$, $-V_{EE} = -10V$, $R_E = 4.7k$, $\beta_{ac} = \beta_{dc} = 100$. Determine with and without $R_E = 200$ the following

- Voltage gain
- Input and output resistances.


Solution : (a) Without R_E

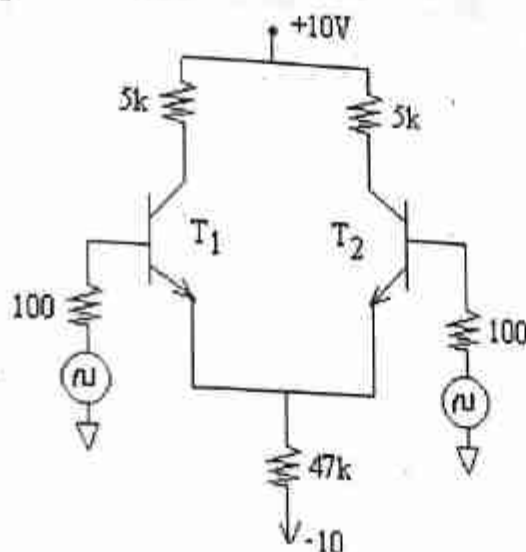

$$I_C = \frac{10 - 0.7}{2R_E + R_i / \beta_{dc}} = \frac{10 - 0.7}{9400 + 100 / 100} = 0.989 \text{ mA}$$

$$r_e = \frac{V_T}{I_C} = \frac{25\text{m}}{0.989\text{m}} = 25.27\Omega$$

$$A_d = \frac{V_o}{V_{id}} = \frac{R_C}{r_e} = \frac{5k}{25.27} = 197.8$$

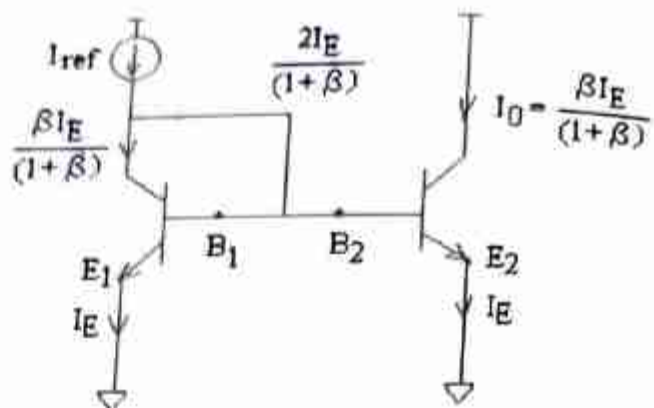Simple Current Mirror circuit :-

$$I_E = (1 + \beta)I_B = I_C + I_B$$


$$I_{ref} = \frac{\beta I_E}{(1 + \beta)} + \frac{2I_E}{(1 + \beta)} = \frac{(2 + \beta)I_E}{(1 + \beta)}$$

$$I_O = \frac{\beta I_E}{(1 + \beta)}$$

$$\frac{I_O}{I_{ref}} = \frac{1}{1 + 2/\beta} \quad \text{for } \beta \gg 2$$

$$I_O \cong I_{ref}$$

β is temperature dependance. In order to avoid temperature dependency upto some extent we improved mirror circuit.

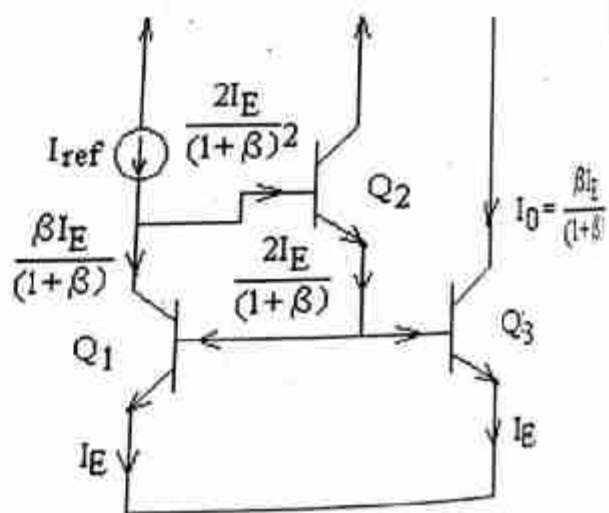Improved Current Mirror circuit :-

$$I_{ref} = \left[\frac{\beta}{1 + \beta} + \frac{2}{(1 + \beta)^2} \right] \cdot I_E$$

$$I_O = \frac{\beta I_E}{(1 + \beta)}$$


$$\frac{I_O}{I_{ref}} = \frac{1}{1 + 2/(\beta^2 + \beta)} \cong \frac{1}{1 + 2/\beta^2}$$

Now here error due to fixed β is reduced from $2/\beta$ to $2/\beta^2$

But in order to achieve better base current compensation and increase output resistance we use other circuits explained below :

OPERATIONAL AMPLIFIER

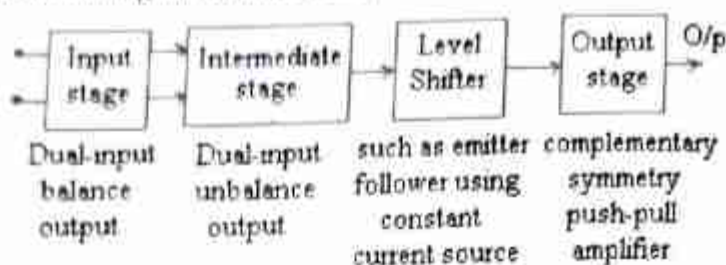The basis of an Op-Amp is a differential amplifier as discussed previously. It is basically a direct coupled amplifier. Its block diagram is shown below :



Input Stage :- It provides almost all the voltage gain of Op-amp and also establish the input impedance of Op-amp.

Intermediate Stage :- It provides remaining gain of Op-amp.


Level Shifting :- Because of the direct coupling d.c. voltage at output is well above the ground level in order to get back the d.c. level to ground potential. So that variation in output is only because of input signal we use level shifting.

Output stage :- It raises the current supplying capability and increases the output voltage swing and this stage's proper design will provide the low output resistance.

Definitions :-

Output Offset Voltage :- Output voltage when both the inputs are grounded is called output offset voltage. It should be zero for ideal voltage.

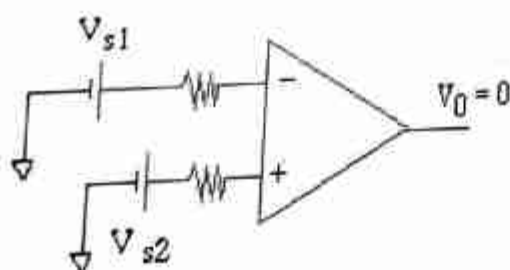
Input Offset Voltage :- The differential input voltage applied at input side to make the output offset voltage zero is called Input Offset Voltage.



$$V_0 = V_{s1} - V_{s2}$$

Input Offset Current :- Algebraic difference between the current of non-inverting and inverting terminals is known as Input Offset Current provided output voltage is zero.

$$I_{io} = |I_{B1} - I_{B2}|$$

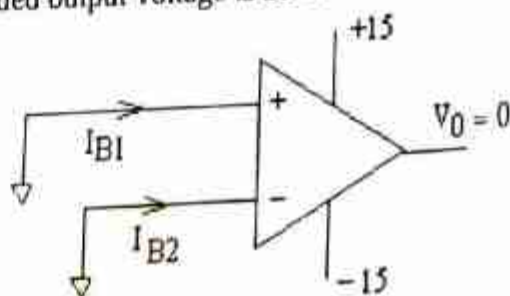

Input Bias Current :- Average of two current that flow through inverting and non-inverting input is known as Input Bias Current provided output voltage is zero.

$$I_B = \frac{I_{B1} + I_{B2}}{2}$$

Power Supply Rejection Ratio :- Change in input offset voltage with power supply variation is Power Supply Rejection Ratio.

$$SVVR = \frac{\Delta V_{io}}{\Delta V_{ii}}$$

Common Mode Rejection Ratio (CMRR) :- It is the most important characteristic of Op-amp. It is defined as the ratio of differential gain to common mode gain.

$$CMRR = \frac{A_d}{A_{CM}}$$

It represents the ability of Op-amp to reject the common mode signal.
For practical Op-amp. Output voltage is given by

$$V_o = A_d \left(V_d + \frac{V_{CM}}{CMRR} \right)$$

A_d = differential voltage gain

V_{CM} = common mode input signal

CMRR = common mode rejection ratio

In order to avoid any common mode amplification CMRR should be infinite which can be achieved

by increasing R_E because $CMRR = \frac{A_d}{A_{CM}}$

and,
$$A_{CM} = \frac{R_C}{2R_E}$$

Question: Find out R_C , R_E and R_{in} for an unbalance differential amplifier when following data are given

$$A_d = 250$$

$$\beta = 2000$$

$$I_{CQ} = 100 \mu A$$

$$CMRR = 74 \text{ dB}$$

Solution : We know,

$$A_d = \frac{R_C}{2r_e}$$

.....(i)

$$r_e = \frac{V_T}{I_{EQ}} = \frac{25m}{100\mu} = 250 \Omega$$

From equation (i)

$$\frac{R_C}{2r_e} = 250$$

$$R_C = 250 \times 2 \times 250 = 125k$$

Given CMMR = 74 dB

$$20 \log \frac{A_d}{A_{CM}} = 74$$

$$\frac{A_d}{A_{CM}} = 5000 \Rightarrow A_{CM} = \frac{250}{5000} = .05$$

$$A_{CM} = \frac{R_C}{2R_E} = .05 \Rightarrow R_E = 1.25 M\Omega$$

$$R_{in} = 2\beta_{ac}r_e \Rightarrow R_{in} = 1 M\Omega$$

Slew Rate :

Maximum rate of change of output voltage w.r.t. time is defined as Slew rate.

$$\left| \frac{dV_o}{dt} \right|_{\max} = \text{S.R.}$$

It represents the how fast output can change with change in the input frequency.
Let output voltage be $= V_m \sin \omega t$


$$\text{Slew rate} = \left| \frac{dV_o}{dt} \right|_{\max} = |V_m \omega|$$

Max. frequency variation is the sinusoidal output depends on $\frac{\text{S.R.}}{V_m 2\pi} = f_{\max}$

Characteristic of Op-amp :

- It should have very high voltage gain.
- It should have very high input resistance.
- It should have very low output resistance.
- Output voltage should be zero, for zero input, i.e. noise should not be amplified.
- It should have very wide B.W. from 0 Hz to MHz.
- CMRR should be very high to avoid any common mode noise at output.
- It should have very high slew rate so that output can follow the input instantaneously.

Equivalent Circuit of an Op-amp :

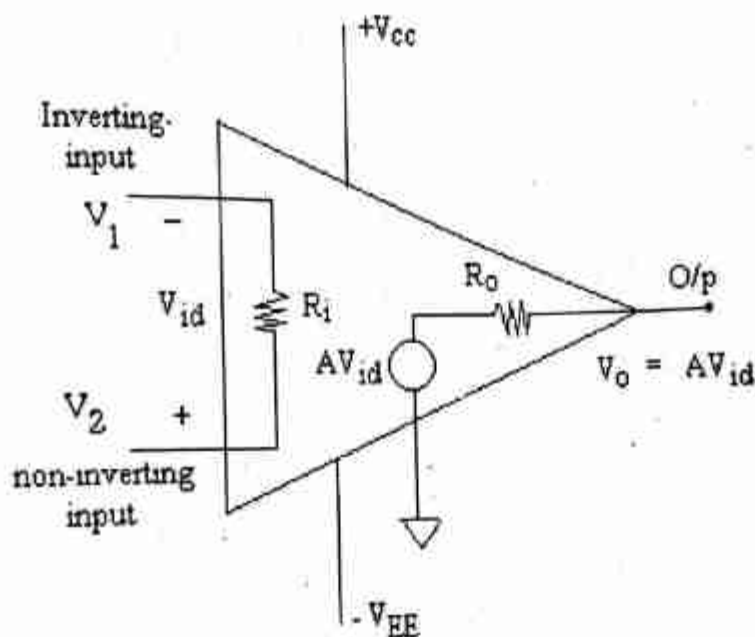


$$V_o = A(V_1 - V_2) = AV_d$$

Virtual Ground :- Since open loop voltage gain A of operational amplifier is infinity,

therefore, $V_d = V_1 - V_2 = \frac{V_o}{A} = 0$

or, $V_1 = V_2$

If non-inverting terminal is connected to ground (i.e. $V_2 = 0$) then inverting terminal voltage also be zero (as $V_1 = V_2 = 0$). This condition is called virtual grounding. Because input resistance is infinite, therefore input is also zero. Virtual Grounding is conceptually different from the actual ground. Input terminal is zero, but it can handle infinite current.

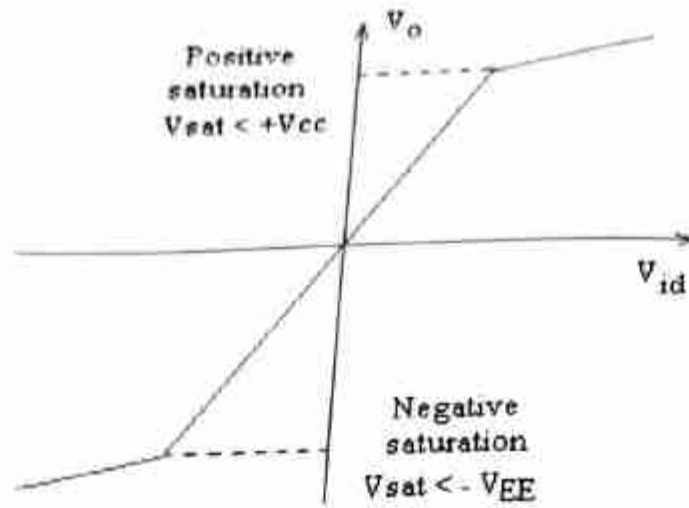Ideal voltage transfer curve :


As we already seen that differential amplifier works as an limiter because $V_{B1} - V_{B2} > \pm V_{BE}$ saturates the transistor as seen from the transfer characteristic of differential amplifier. Hence ideal voltage transfer curve of Op-amp also saturates at positive and negative saturation level.

This characteristic is very useful in sine to square wave conversion.

Open loop configuration :


When there is no direct or indirect connection from output to input then the configuration are called open loop configuration.

There are three open loop configurations :

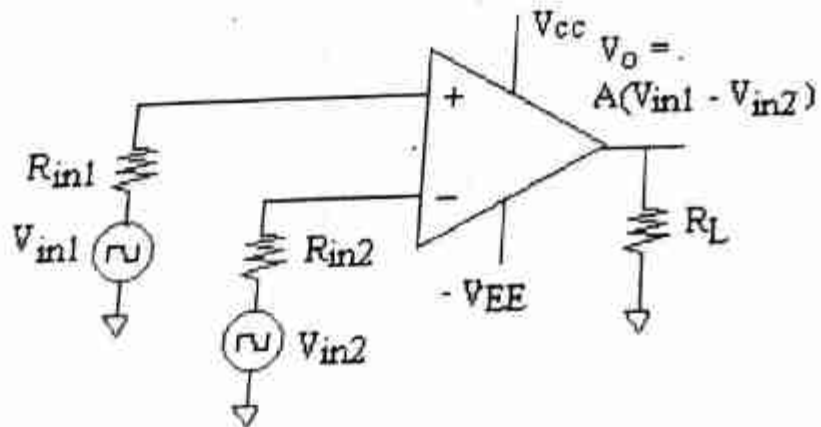The differential amplifier :-

= open loop gain


Inverting amplifier :-

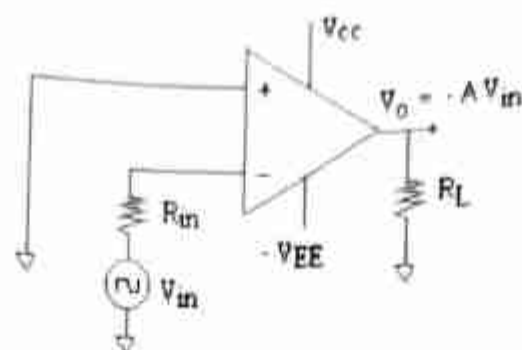

$$V_i = -A V_{in}$$

180° phase shifter

The Non-inverting amplifier :-

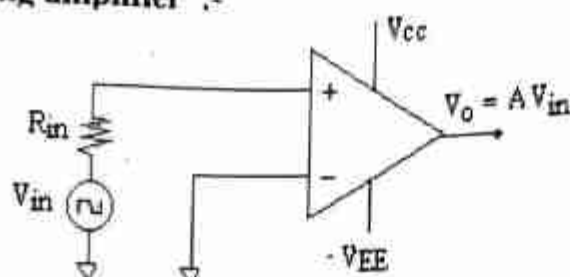

In all three open loop configuration the open loop gain is so high that even any differential input slightly greater than zero volt drives output to saturation level. Therefore the Op-amp works as comparator rather than working as amplifier. This is the reason why the open loop Op-amp are not preferred in linear application however it has few of its unique advantages

Advantage of Open loop Op-amp :

It has very high voltage gain which makes open loop configuration more susceptible to noise. Because of such a high voltage gain op-amp always works on saturation mode even though the input signal is very small.

Bandwidth of open loop op-amp is negligibly small. (Gain \times Bandwidth = constant)

In order to sort out the problem listed above. We use feedback configuration.

Types of feedback :-

Positive or regenerative feedback.

Negative or degenerative feedback.

Negative feedback is of our concern here because of numerous advantages. It has at the cost of loss in gain which is also advantageous in Op-amp.

Negative feedback may be of four type as already discussed in feedback section.


1. Voltage series
2. Voltage shunt
3. Current series
4. Current shunt

Mode of operation with negative feedback :-

As far as Op-amp is concerned there are three mode of operation with negative feedback

1. Inverting mode.
2. Non-inverting mode.
3. Differential mode.

1. Inverting mode :-

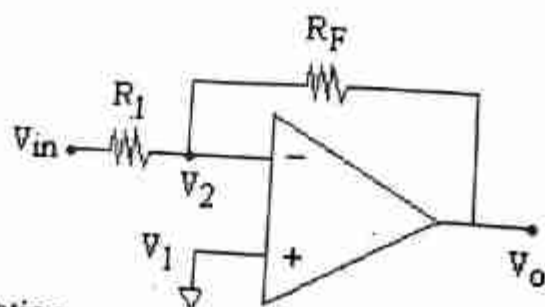


It is a voltage shunt configuration.

$$\frac{V_{in} - 0}{R_1} = \frac{0 - V_o}{R_F} \text{ using virtual ground concept}$$

$$\frac{V_o}{V_{in}} = -\frac{R_F}{R_1}$$

$$A_{VF} = \frac{V_o}{V_{in}} = -\frac{R_F}{R_1}$$

Non-inverting mode :-

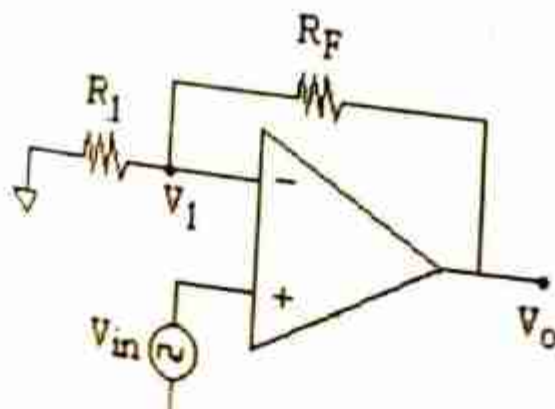


$$V_1 = V_{in}$$

at V_1

$$\frac{V_{in}}{R_1} = \frac{V_{in} - V_0}{R_F} \Rightarrow \frac{V_0}{V_{in}} = \left(1 + \frac{R_F}{R_1} \right)$$

Differential mode :-

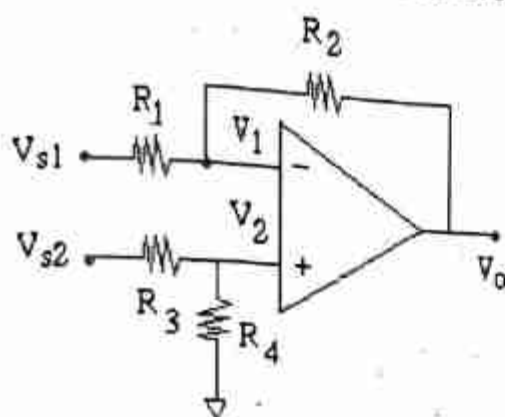Circuit of differential amplifier (also sometimes called subtractor) is given below :



Output voltage is given by, $V_0 = V_{o1} + V_{o2}$ (i)

V_{o1} is the voltage due to V_{s1} when $V_{s2} = 0$

$$V_0 = V_{s2} + V_{o2}$$

$$V_{o1} = -\frac{R_2}{R_1} V_{s1} \quad \text{.....(ii)}$$

V_{o2} is the voltage due to V_{s2} when $V_{s1} = 0$

$$V_{o2} = V_2 \left(1 + \frac{R_2}{R_1} \right) \quad \text{and} \quad V_2 = \frac{R_4}{R_4 + R_3} V_{s2}$$

$$V_{o2} = V_{s2} \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4}{R_4 + R_3} \right) \quad \text{.....(iii)}$$

From equation (i), (ii) and (iii)

$$V_0 = V_{o1} + V_{o2} = V_{s2} \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_4}{R_4 + R_3} \right) - \frac{R_2}{R_1} V_{s1} \quad \text{.....(iv)}$$

$$R_2 = R_4 \quad \text{and} \quad R_3 = R_1$$

$$V_0 = \frac{R_2}{R_1} (V_{s2} - V_{s1})$$

$$(ii) \quad R_3 = R_1$$

$$V_o = V_{o1} = V_{o2}$$

Common Mode :

If $V_{o1} = V_{o2}$, $V_o = 0$. This is called common mode. This mode is helpful to reject noise which is same at both the input terminals.

Common Mode Rejection Ratio (CMRR) :

$$\text{Common mode signal, } V_c = \frac{V_{s1} + V_{s2}}{2}$$

$$\text{Differential signal } V_d = V_{s2} - V_{s1}$$

Then from equation (v) and (vi)

$$V_{s1} = V_c - \frac{V_d}{2}, \quad V_{s2} = V_c + \frac{V_d}{2}$$

Now substituting the value of V_{s1} and V_{s2} in equation (iv)

$$V_o = V_c \left[\left(\frac{R_1 + R_2}{R_3 + R_4} \right) \frac{R_4}{R_1} - \frac{R_2}{R_1} \right] - \frac{V_d}{2} \left[\left(\frac{R_1 + R_2}{R_3 + R_4} \right) \frac{R_4}{R_1} + \frac{R_2}{R_1} \right]$$

$$A_d = \frac{V_o}{V_d} \bigg|_{V_c=0} \quad \text{and} \quad A_{CM} = \frac{V_o}{V_c} \bigg|_{V_d=0}$$

$$\text{and } CMRR = \frac{A_d}{A_{CM}} = \frac{\frac{1}{2} \left[\left(\frac{R_1 + R_2}{R_3 + R_4} \right) \frac{R_4}{R_1} + \frac{R_2}{R_1} \right]}{\left[\left(\frac{R_1 + R_2}{R_3 + R_4} \right) \frac{R_4}{R_1} - \frac{R_2}{R_1} \right]}$$

Condition for maximum CMRR :

To obtain $CMRR = \infty$, common mode gain should be zero.


$$A_{CM} = \left(\frac{R_1 + R_2}{R_3 + R_4} \right) \frac{R_4}{R_1} - \frac{R_2}{R_1}$$

if, $R_3 = R_1$ and $R_4 = R_2$ then $A_{CM} = 0$

APPLICATIONS OF OP-AMP *only remember*

Op-amp can be used as Summing, Scaling and Averaging Amplifiers.

Summing amplifier

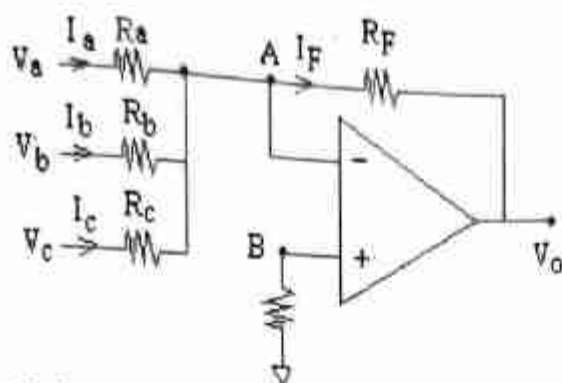

Considering Op-amp ideal.

$$I_a + I_b + I_c = I_F \quad \dots (i)$$

Voltage at node B is zero therefore by using virtual ground concept voltage at node A is also 0 volt.
Equation (i) can be written as

$$\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} = -\frac{V_o}{R_F}$$

$$V_o = -R_F \left(\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} \right)$$

Averaging amplifier :

$$\text{If } R_1 = R_2 = R_3 = 3R_F \quad V_o = \left(\frac{V_a + V_b + V_c}{3} \right)$$

Comparator :


$$\text{If } R_a = R_b = R_c = R_F \quad V_o = -(V_a + V_b + V_c)$$

Scaling amplifier :

$$V_o = -\left(\frac{R_F}{R_a} V_a + \frac{R_F}{R_b} V_b + \frac{R_F}{R_c} V_c \right) \quad \frac{R_F}{R_a} \neq \frac{R_F}{R_b} \neq \frac{R_F}{R_c}$$

by selecting proper values of $\frac{R_1}{R_a}$, $\frac{R_1}{R_b}$, $\frac{R_1}{R_c}$ proper weighted might be given to each.

Non-inverting amplifier :

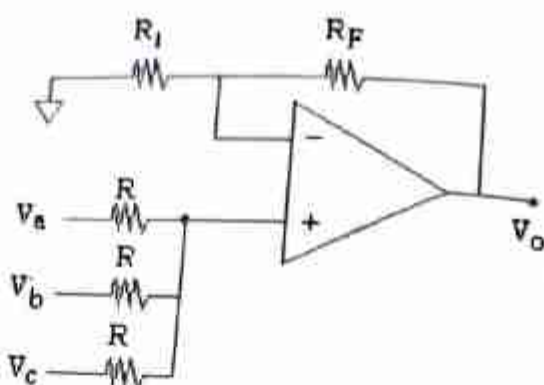

$$V_o = -\left(1 + \frac{R_F}{R_1}\right) \left(\frac{V_a + V_b + V_c}{3}\right)$$

Averaging amplifier :

It is a averaging which is amplifying the average of three signal by gain $\left(1 + \frac{R_F}{R_1}\right)$.
 making $\left(1 + \frac{R_F}{R_1}\right) = 1$. The circuit will work as averager.


number :

By making $\left(1 + \frac{R_F}{R_1}\right) = 3$

i.e. $R_F = 2R_1$ the circuit provides sum of three input signal.

$$V_o = V_a + V_b + V_c$$

Factor 1

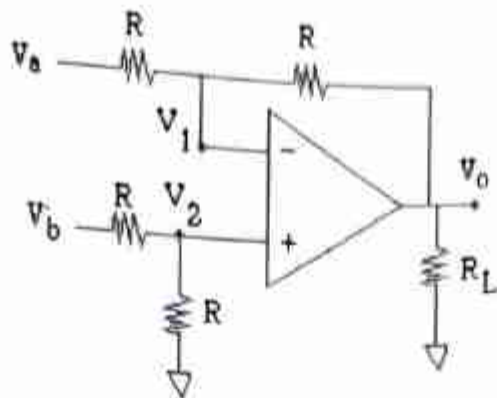


$$V_o = -V_a + V_2 \left(1 + \frac{R}{R}\right) \quad \text{and} \quad V_2 = \frac{V_b R}{R + R} = \frac{V_b}{2}$$

$$V_o = -V_a + \frac{V_b}{2} \left(1 + \frac{R}{R}\right) \quad V_o = V_b - V_a$$

circuit provides subtraction of two circuits.

Integrator :

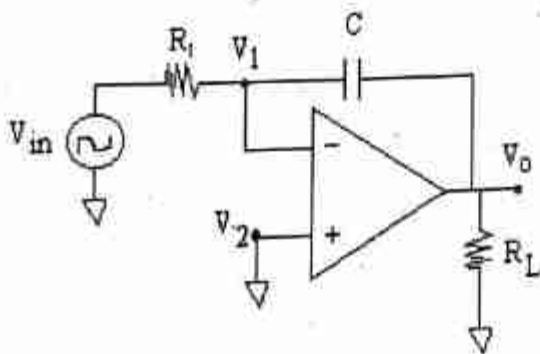

$$V_2 = 0$$

at node V_1

$$\frac{-0}{R_i} = C \frac{d(0 - V_o)}{dt}$$

$$\frac{V_m}{R_i} = -C \frac{dV_o}{dt}$$

$$= -\frac{1}{R_i C} \int V_m dt$$

$$T > R_i C_f$$

proper functioning of Integrator $T > R_i C_f$


- T = Time period of signal
 $R_1 C$ = Time constant of integrator.

Limitations :


1. In the absence of input voltage the Op-amp will work on open loop Op-amp and shows towards noise.
2. It also has low frequency Roll off problem

Practical Op-amp :

Both the limitations can be corrected by using, practical op-amp

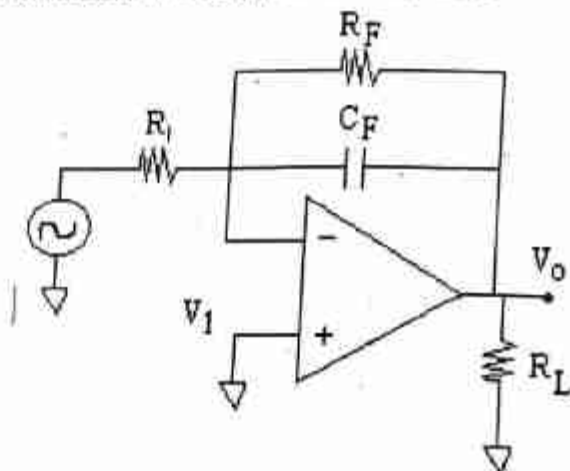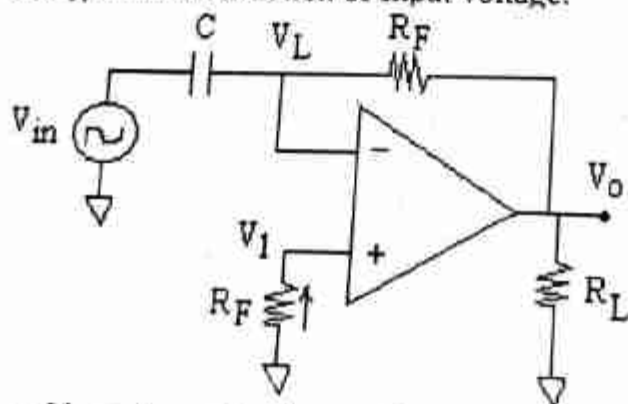**Differentiator :-**

Output voltage is differentiation of Input voltage.



$$V_1 = V_2 = 0 \quad \text{virtual ground}$$


$$V_o = -R_F C \frac{dV_m}{dt}$$

Limitation :-

Above differential amplifier has higher frequency noise, sensitivity, high frequency noise spikes at the output.

Practical differentiator :-

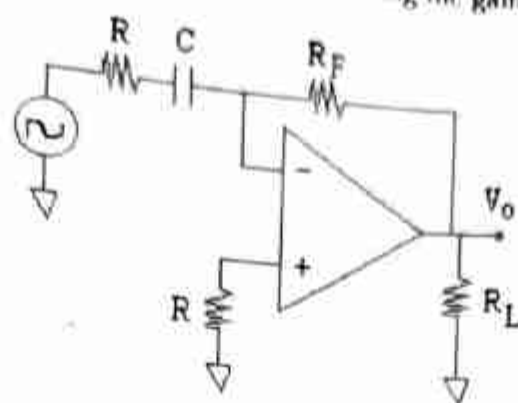Practical differentiator reduce the high frequency noise significantly.
Practical differentiator provides more stability by preventing the gain to be very high at high frequency.



$$T > R_F C$$


T = Time period of signal

$R_F C$ = Time constant of differentiator.

Other important Linear Op-amp circuit :


Double Integrator :-
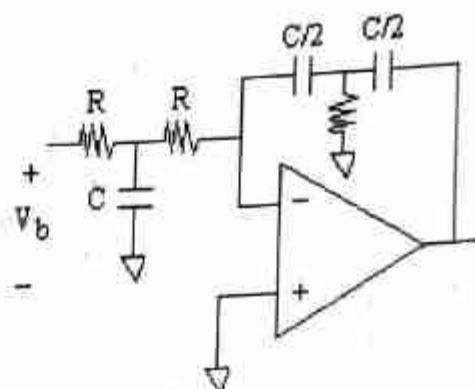
$$V_o = \frac{-4}{(RC)^2} \iint V_i dt dt$$




Current amplifier :-
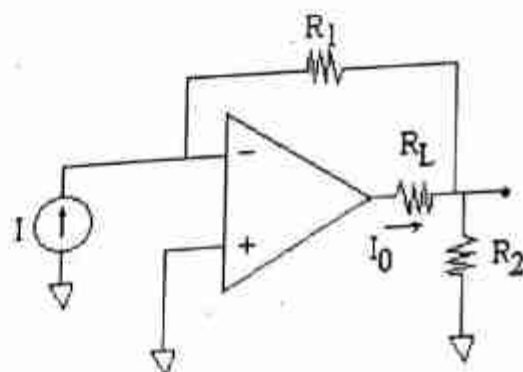
$$\frac{I_o}{I} = -\left(\frac{R_1}{R_2} + 1\right)$$




3. Floating load voltage to current convertor :-

$$I_L = \frac{V_s}{R_1}$$

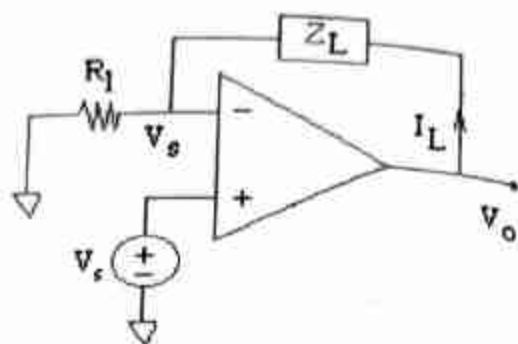


4. Grounded load voltage to current convertor :-

$$I_L = \frac{V_s}{R_2}$$

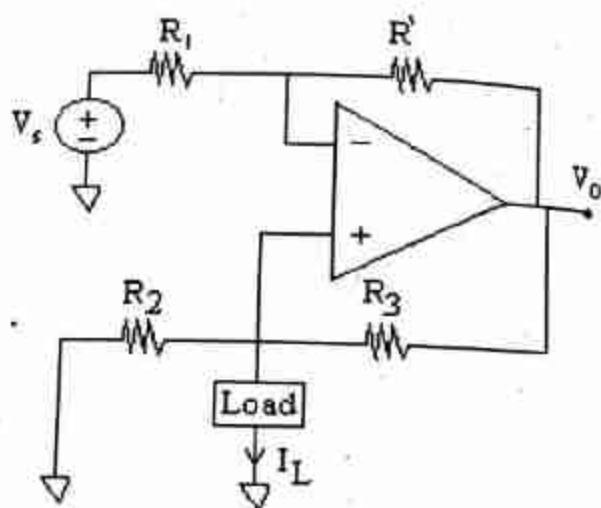


5. Current to voltage convertor :-

$$V_o = -I_s R_F$$

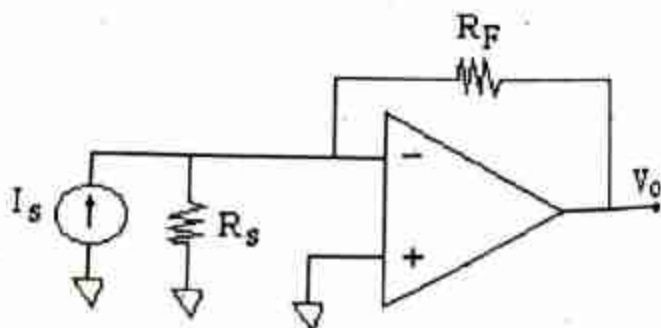

Instrumentation amplifier :-
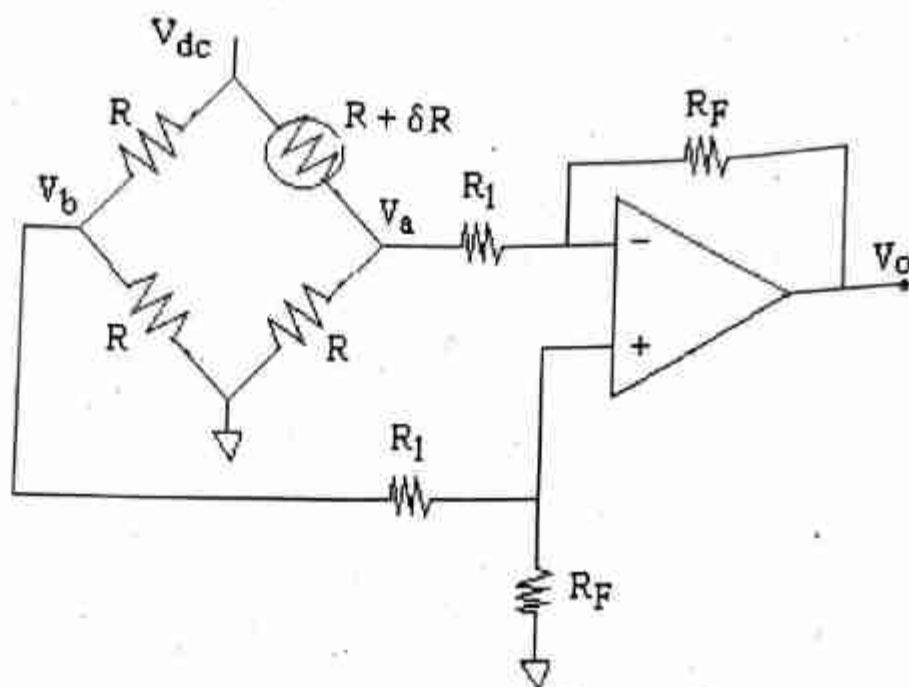
$$= \frac{R_F}{R_1} \cdot \frac{\delta R}{4R} V_{dc}$$



filters :

passes or reject the band of frequency and reject or pass the all other frequencies.

Advantages of active filter over passive

1. Bandwidth and frequency adjustment is available.

2. High input and low output impedance therefore it does not suffer from loading problem.

3. Active filters are cheaper than the passive filter.

4. Active filter does not require inductor.

Types of filter

1. Low-pass filter (passes a band of frequency up to a highest frequency)

2. High-pass filter (passes all frequencies higher than specific frequency)

3. Band-pass filter (passes a band of frequency in mid range)

4. Band-stop filter (rejects a band of frequency in mid range)

5. All-pass filter (passes all the frequencies)


Active filters are of following types :

1. Butterworth Filter :- It has flat pass band and flat stop band.

Pass filter :

All pass filters pass all the frequency without any attenuation, while providing predictable phase shift for the different frequencies of input signal.
All pass filter is used as a phase corrector or delay equalizers.
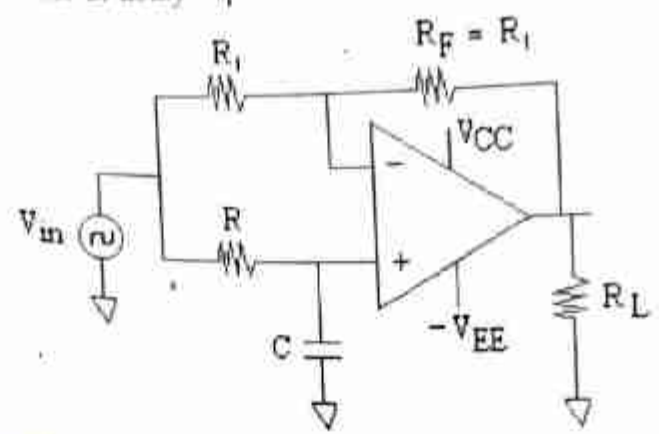
$$V_o = \frac{1 - j2\pi f_R C}{1 + j2\pi f_R C} V_m$$



Phase shift $= \phi = -2 \tan^{-1}(2\pi fRC)$

with interchanging the position of R and C we can achieve positive phase variation.

Linear Applications of Op-amp

Comparator :-


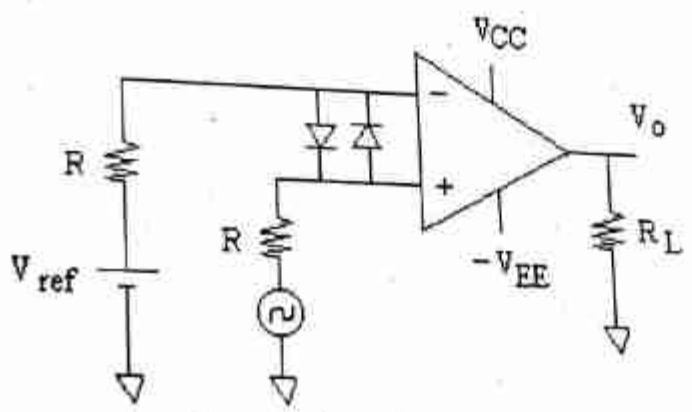



fig. non-inverting comparator.

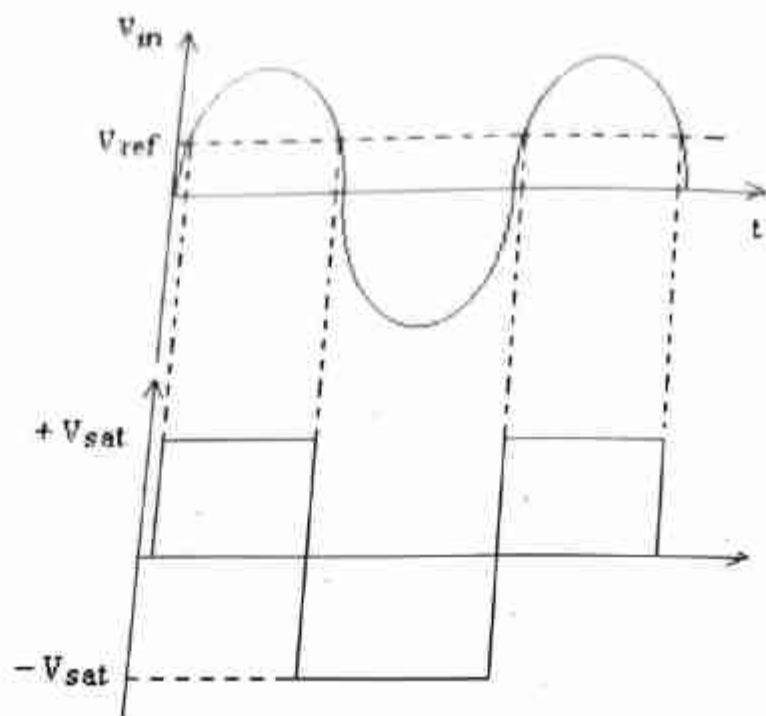Comparator is a circuit which compares the input signal with reference signal and gives output as either $+V_{sat}$ or $-V_{sat}$ as per the comparison of signals.




Zero Crossing Detector :-

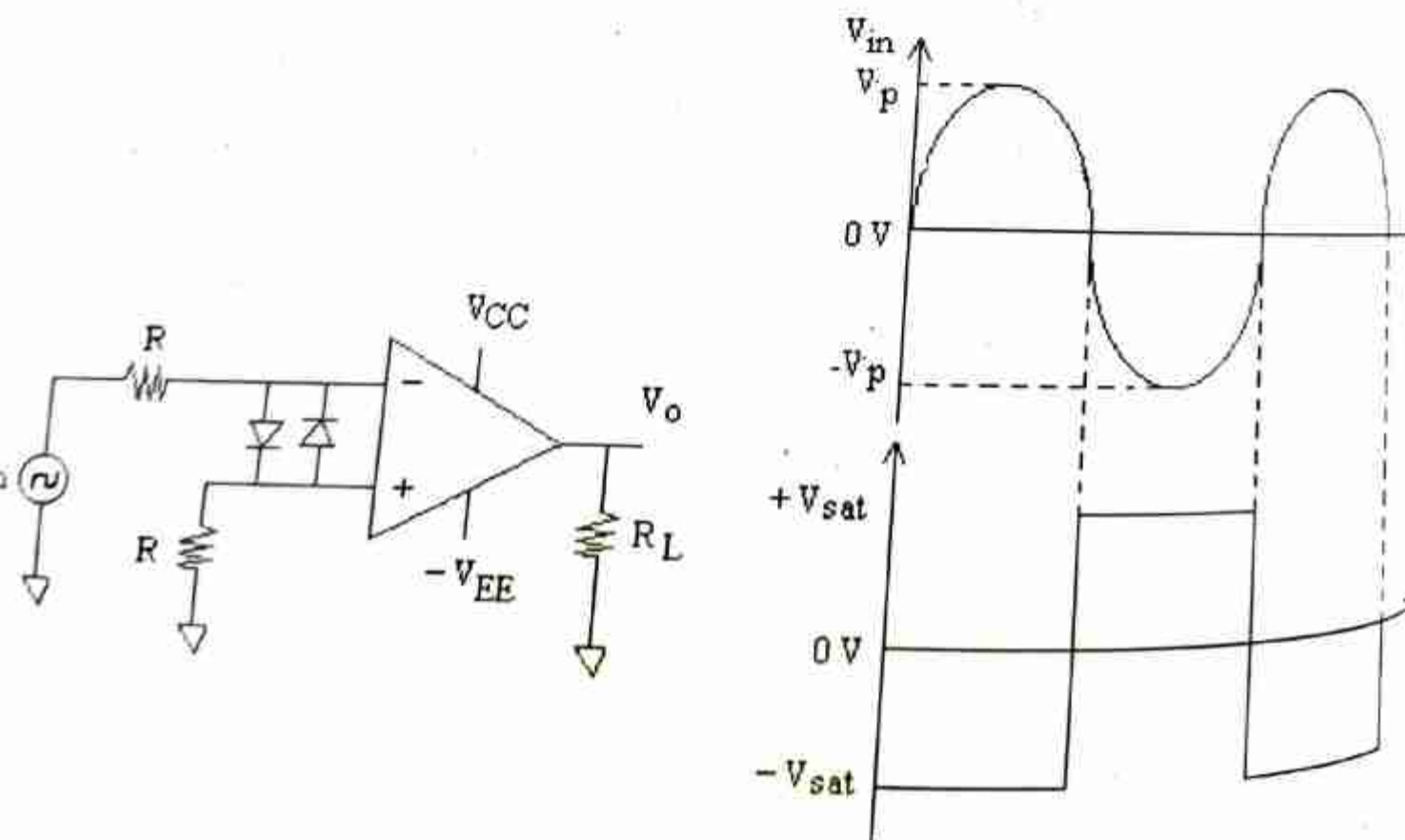You might say the zero crossing detector in application of comparator in which the transition of output voltage from $+V_{sat}$ to $-V_{sat}$ or vice versa take place. Whenever the input signal crosses the zero level.



and Hold Circuit :-

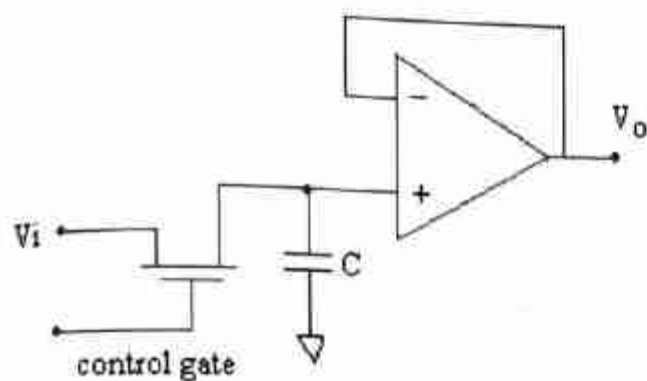

providing proper control negative pulse at control gate. We take the sample at input signal and hold the same value for a while.

Rectifiers :-

A diode can rectify the signal that must be greater than 0.7 V. In order to rectify the signal at precision rectifiers are used.

precision rectifier :-

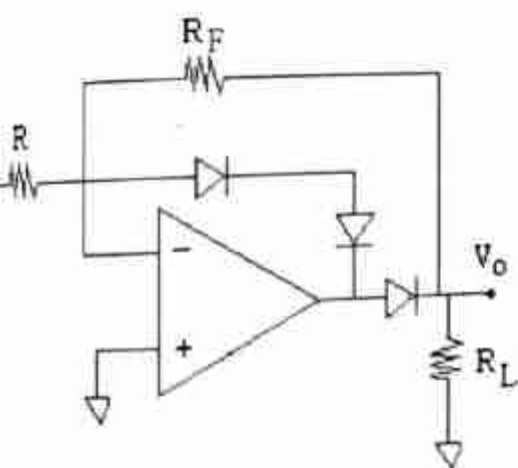


Fig. Circuit of half wave rectifier.

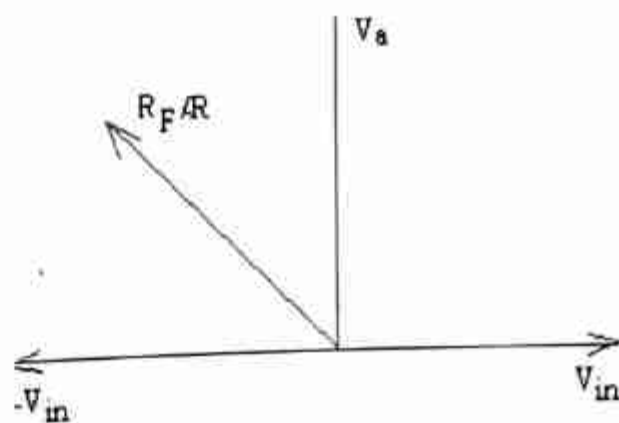


Fig. Transfer characteristic

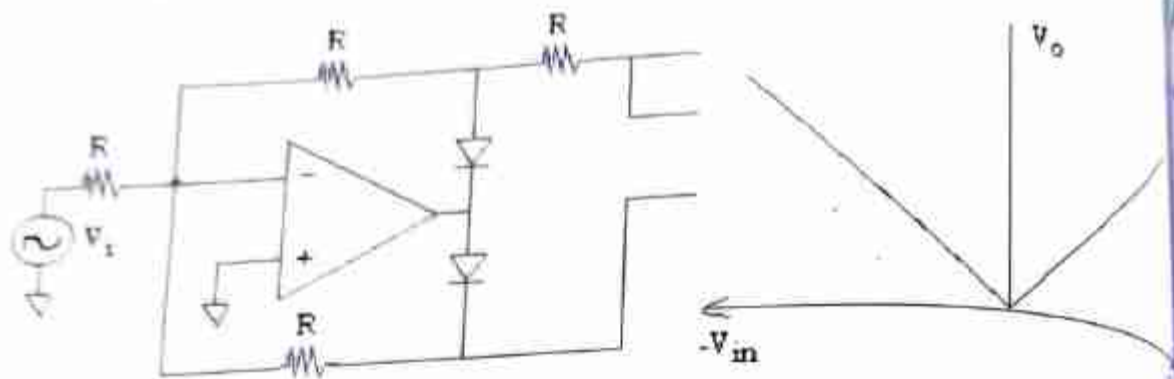
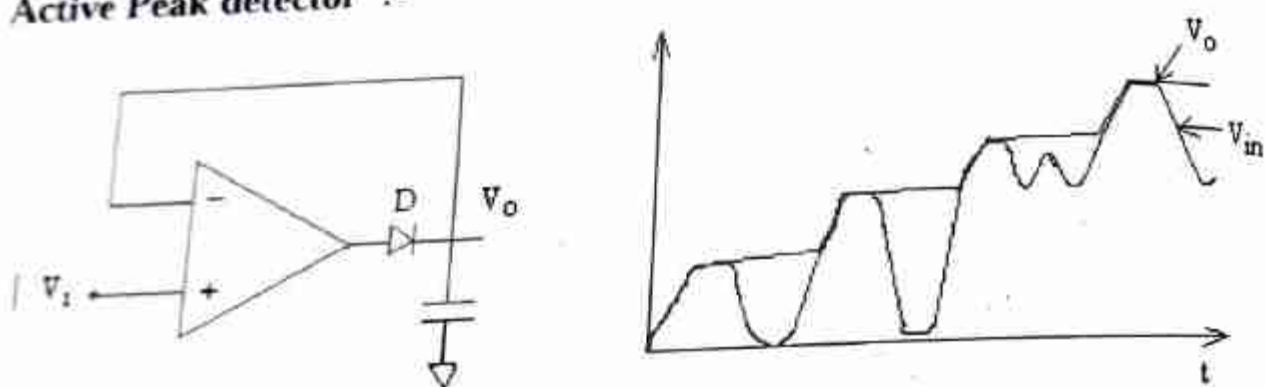
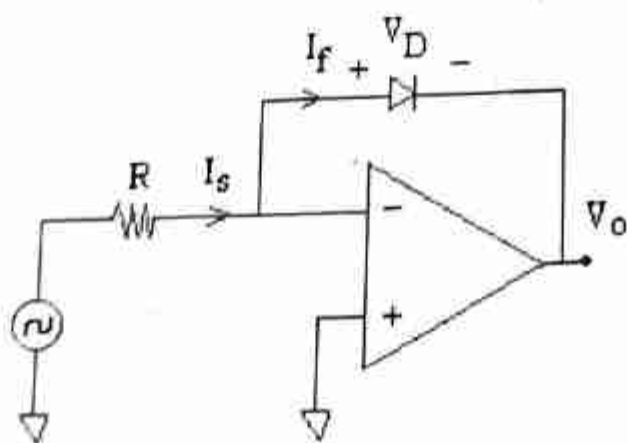
Full wave rectifier :-

Fig. Circuit of full wave rectifier.

Transfer characteristic.

Active Peak detector :-

It detects the peak of the input signal and does not follow the instantaneous variation of the signal.

Logarithmic amplifiers :-


In logarithmic amplifier the output is the log of input.

$$V_o = -V_T \ln \frac{V_i}{I_s R}$$

Antilog Amplifier :-

It performs exactly opposite function of logarithmic amplifier. It provides the antilog of input at

$$V_D = -RI_s \ln^{-1} \frac{V_i}{V_T}$$

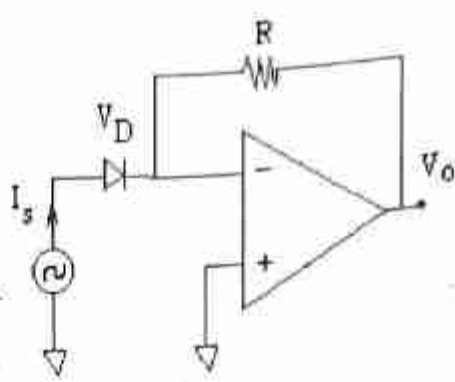

Schmitt Trigger :-

Schmitt trigger circuit is a positive feedback circuit which converts any irregular wave into square

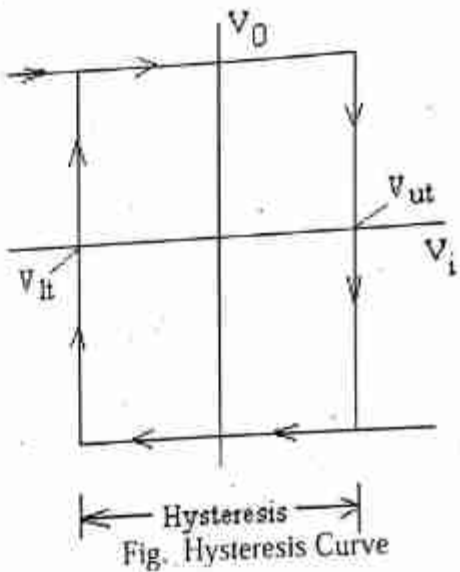
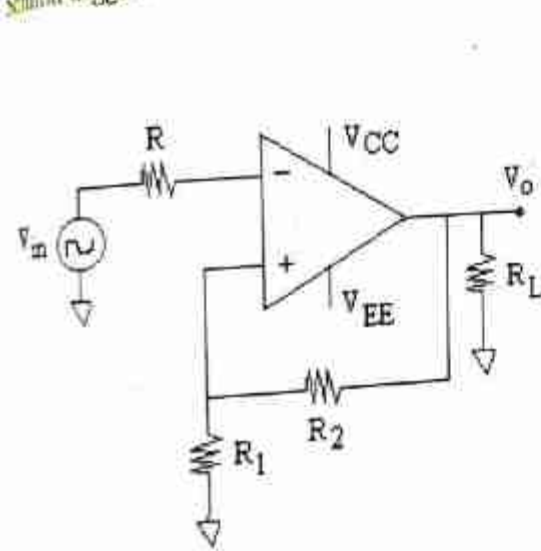


Fig. Inverting Schmitt Trigger

Figure shows the circuit arrangement of inverting Schmitt trigger.

It has two threshold level which are decided by the voltage divider feedback made by R_1 and R_2

$$V_{ut} = \frac{R_1}{R_1 + R_2} (+V_{sat}) \quad V_{lt} = \frac{R_1}{R_1 + R_2} (-V_{sat})$$

when the V_{in} is greater than V_{ut} the output changes from $+V_{sat}$ to $-V_{sat}$ and with $V_{in} < V_{lt}$ output changes from $-V_{sat}$ to $+V_{sat}$

Hysteresis voltage is given by

$$V_H = V_{ut} - V_{lt}$$