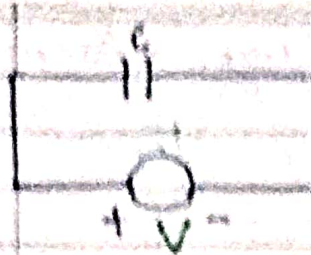


RC CIRCUIT

$$V_c = \frac{1}{C} \int i dt$$

$$i = C \frac{dV_c}{dt}$$

If cap. fully charged.
flow of any more electrons
onto its plates, as it becomes
saturated.




when ac applied to
circuit, it holds voltage
across it.
Here current is opposed by
the any changes in the
voltage at a rate which is
equal to the rate of change
of the electrom. charges in
the plates.

AC Through capacitor.


ac. circuit cap. constantly charging & discharging. This
± changes in saturation of voltage takes time to deposit
or release charges.

$I = \text{max.}$

case I.
S.C.

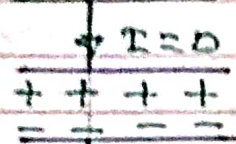


case-II.

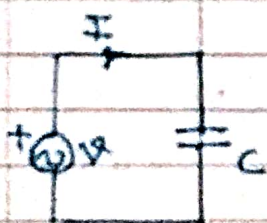

$$V = V_m \sin \omega t$$

$$i_c = C \frac{dV_c}{dt}$$

I_c

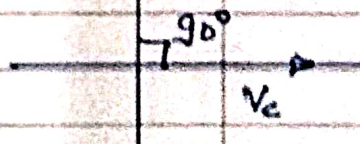

rate of change
 V_c across the plates
is known at its max.
 i_c = also maximum.
Hence Max. amount of
electrons are moving
from one plate to another
 I_c phase Lead V_c phase
when plates saturated no current
flows.

case III


$I(\text{max})$

polarity reversed.

$I = 0$

case IV.



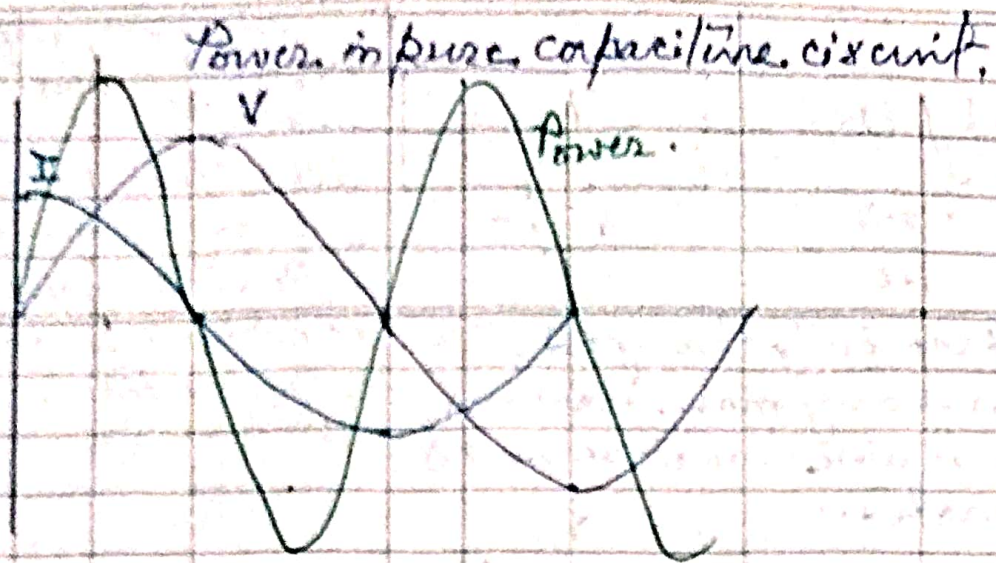

Instantaneous power (at any time).

$$P = V_m \sin \omega t \cdot I_m \sin(\omega t + 90^\circ)$$

$$= V_m I_m \cdot \sin \omega t \cdot \cos \omega t$$

$$= V_m I_m \cdot \frac{2}{2} \sin \omega t \cdot \cos \omega t$$

$$= \frac{V_m I_m}{2} \cdot \sin(2\omega t)$$


$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cdot \sin(2\omega t)$$

$$= V_{rms} \cdot I_{rms} \sin(2\omega t)$$

Positive power
energy stored

Negative power
energy released.
average power
in pure capacitor
is zero.

AC FUNDAMENTAL

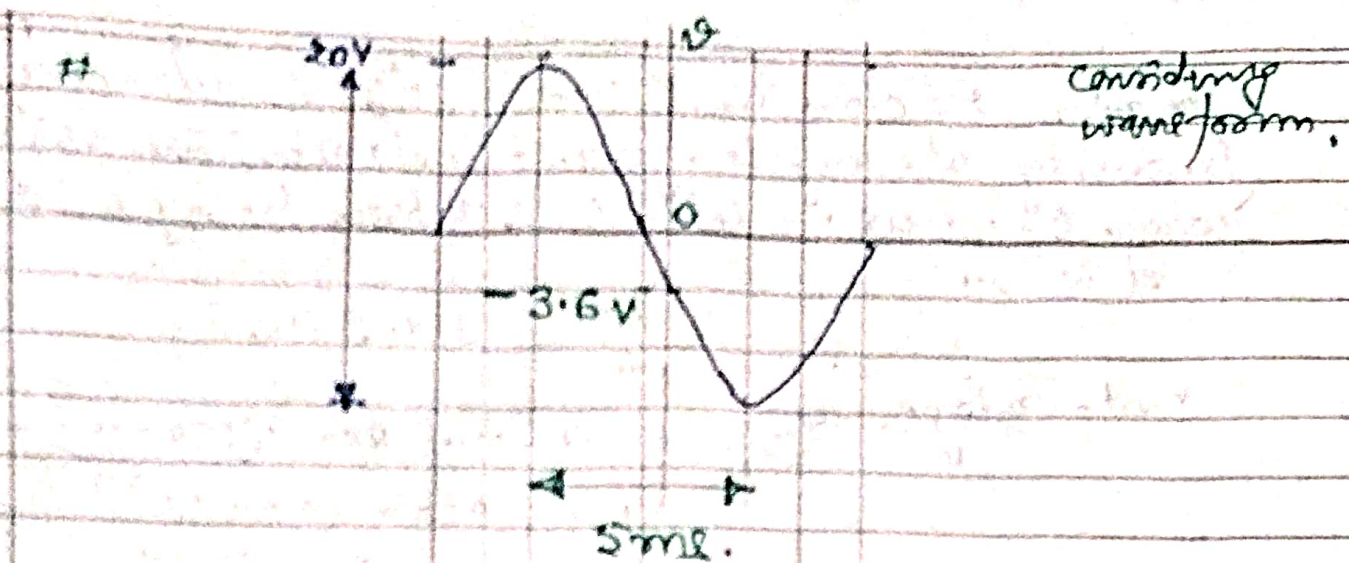

a sinusoidal voltage is 20V r.m.s. has a time betⁿ two cons. p. = 5ms.

5ms. between consecutive 'Peak - ~~Trough~~' ^{Zero} through at $t=0$; voltage is $(-3.6V)$

Find the voltage and value of the voltage at $t=12ms$.

$$V_m = \frac{20}{\sqrt{2}} = 10\sqrt{2}$$

$$T = 2 \times 5ms = 10ms \text{ for one complete cycle.}$$

$$f = \frac{1}{T} = \frac{1}{10ms} = 10^{-3} \times (0.1) = 100\text{ Hz}$$

$$\text{angular freq} = \omega = 2\pi f = 2\pi(100) = 200\pi \text{ rad/s.} \\ = 628.3 \text{ rad/s.}$$

sinusoidal voltage.

$$v(t) = V_m \sin(\omega t + \phi)$$

$$= 10 \sin(628.3 t + \phi)$$

Let $\phi = ?$ Let from fig.

$$\text{at } t=0 \quad v = -3.6 \text{ volt.}$$

$$-3.6 = 10 \sin \phi$$

$$\frac{-3.6}{10} = \sin \phi$$

eg.

$$\phi = \sin^{-1}(-0.36) \\ = -158.9^\circ$$

$$v(t) = 10 \sin(628.3 t - 158.9^\circ)$$

at 12ms value of voltage.

$$v(12ms) = 10 \sin(628.3(0.012) - 158.9^\circ) = 10 \sin(7.54 - 158.9^\circ) = 10 \sin(273.1^\circ) = -2.985 \text{ V}$$

A.C. FUNDAMENTALS.

equation $v = 0.04 \sin(2000t + 60^\circ)$ V, determine the frequency, the angular freq. & instantaneous voltage when $t = 160 \mu s$. what is time represented by 60° of angle.

Let $\omega = 2\pi f$

$$f = \frac{\omega}{2\pi} = \frac{2000}{2\pi} = 318.3 \text{ Hz.}$$

Inst. voltage $V(t) = 0.04 \sin(2000 \cdot (160 \times 10^{-6}) + 60^\circ)$
 $= 0.04 \sin(0.32 \text{ rad} + 60^\circ)$

from eq. $= 2000t$
 $= \omega t \text{ rad.}$

$$= (2000 \times 160) / 10^6 = 0.32$$

Let 0.32 rad into degree.

$$1 \text{ rad} = 180^\circ$$

$$1 \text{ rad} = \frac{180}{\pi}$$

$$0.32 \times \frac{180}{\pi} = 18.32^\circ$$

$$V = 0.04 \sin(18.32^\circ + 60^\circ) \text{ V}$$


$$= 0.04 \sin(78.32^\circ)$$

$$= 0.04 \times (0.98) = 0.0392 \text{ volt.}$$

$$= 39.2 \text{ mV}$$

time period $= T = \frac{1}{f} = \frac{1}{318.3}$

$$= 3.14 \text{ ms.}$$

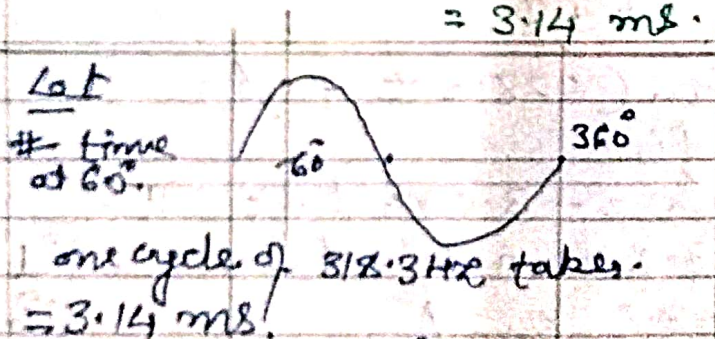

$$t = \frac{60^\circ}{360^\circ} \times 3.14 \text{ ms}$$

$$= 0.52 \text{ ms.}$$

$$\# \quad 2 \text{ rad} = \frac{360^\circ \times 2}{\pi}$$

$$0.32 \text{ V} = 114.6^\circ$$

$$2\pi \text{ rad} = 360^\circ$$

$$\# \quad \frac{7\pi}{4} \text{ rad} \rightarrow \text{degree.}$$

$$\frac{7\pi \times 180}{4 \times \pi} = 315^\circ$$


$$\# \quad \frac{1}{3\pi} \text{ rad} \rightarrow \text{degree}$$

$$\frac{1}{3\pi} \times \frac{180}{\pi} =$$


$$\frac{1}{3\pi} \times \frac{180}{\pi}$$

AC fundamental,


PHASE & PHASE DIFFERENCE

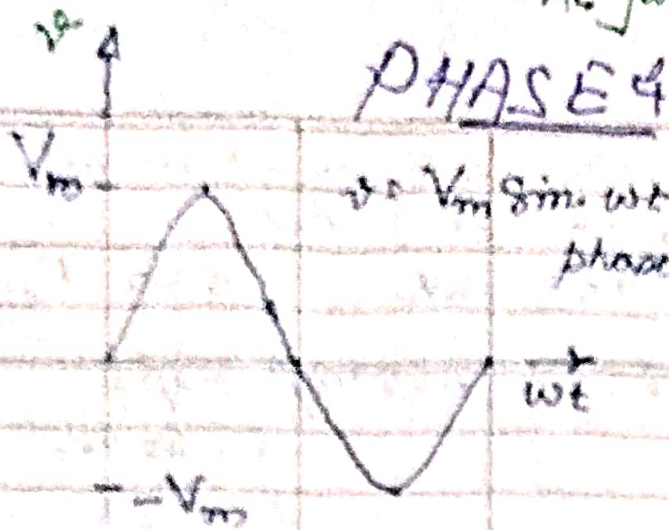

phase shift $\phi = 0^\circ$ Here.


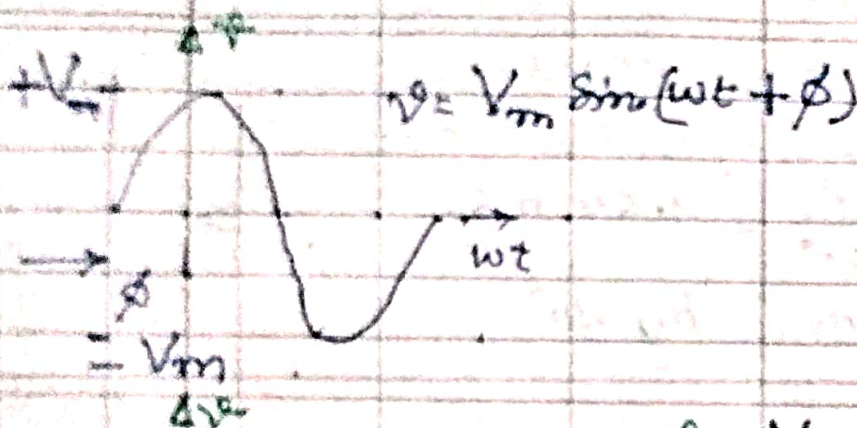


$v = V_m \sin(\omega t - \phi)$ delayed

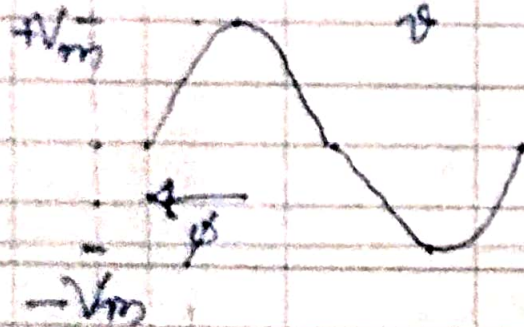

$$v = V_m \sin(\omega t - 90^\circ)$$

$$v = -V_m \sin(\omega t + 180^\circ)$$

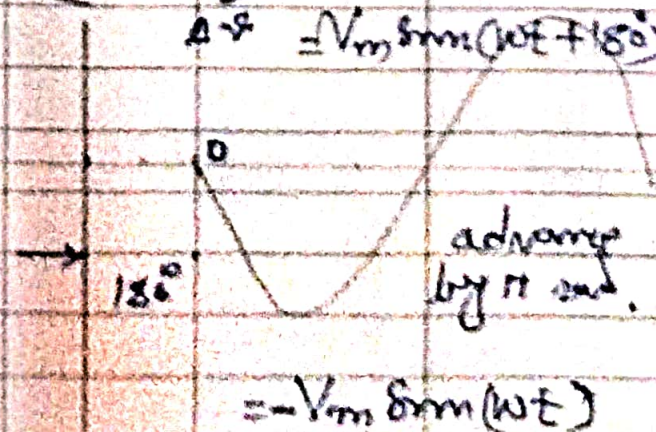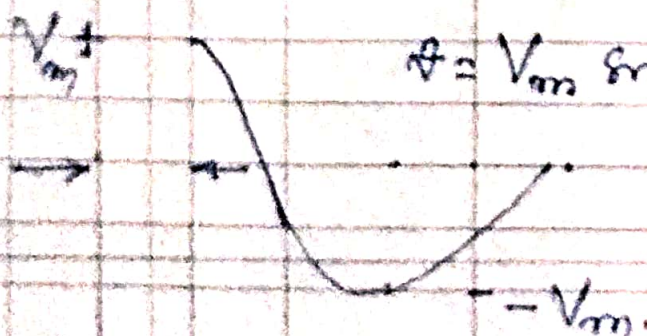

Determine The phase difference of The sinusoidal current $i_1 = 4.8 \sin(100\pi t + 30^\circ)$ Amp

with $i_2 = 6.8 \sin(100\pi t)$ Amp. draw phasor diagram.

$$i_1 = 4.8 \sin(100\pi t + 30^\circ)$$

$$\omega = 100\pi = 2\pi f$$

Let

$$f = 50 \text{ Hz}$$

$$i_2 = 6.8 \sin(100\pi t)$$

$$\frac{1}{f} = T = \frac{1}{50} = 0.02 \text{ Sec} = 20 \text{ ms.}$$

$$100\pi = \omega = 2\pi f$$

$$\text{Hz, } 50 = f = \frac{1}{T} = 20 \text{ ms.}$$

both are same time for full revolution.

$$t = 20 \text{ ms} \cdot \frac{30^\circ}{360^\circ} = 1.67 \text{ ms.}$$

phasor i_1 lead phasor i_2 by 30°

