
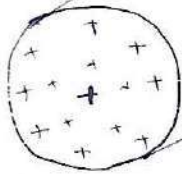



- SKIN EFFECT.

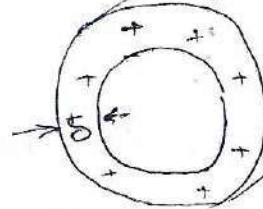

DC



g
CH. 12

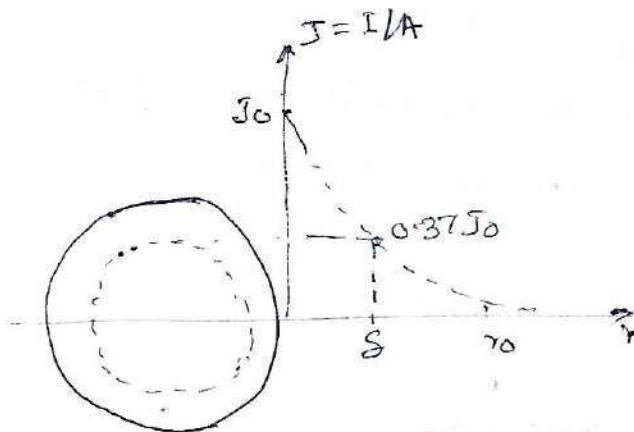

$$R = \frac{2L}{A}$$

At

Consider Cu as cond. medium, what is skin depth
at 60 Hz & 1 MHz

$$\mu = 4\pi \times 10^{-7} \text{ H/m.}$$

$$\sigma = 5.8 \times 10^7 \text{ S/m.}$$


$$\text{At } f = 60, \quad \delta = 0.85 \text{ cm.}$$

$$1 \text{ MHz} \quad \delta = 0.007 \text{ cm.}$$

Skin depth (δ): Current density falls off exponentially from surface of conductor towards center.
At Critical depth (δ) called as skin depth or depth of penetration, signal amplitude is $1/e$ or 36.8% of its surface amplitude.

$$S = \frac{1}{\sqrt{\pi f \mu \sigma}}$$

Scattering Parameters

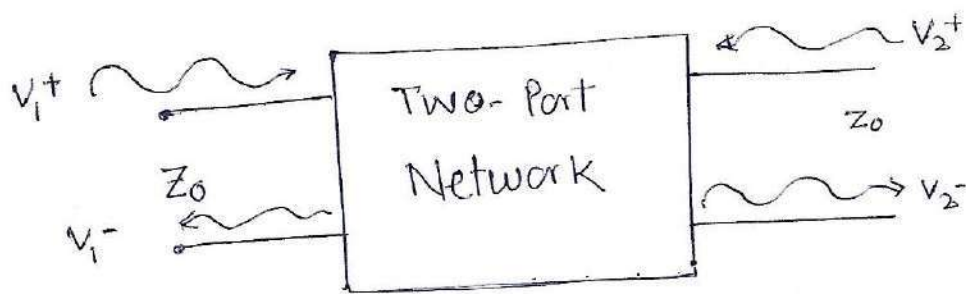

To define the S-parameters accurately, we will consider a voltage phasor $[V_1^+]$ incident on & a voltage phasor $[V_1^-]$ reflected from the terminals of two-port network ($i=1,2$) as shown in Fig.

The Scattering matrix is now defined to describe the linear relationship b/w incident voltage wave phasor matrix $[V^+]$ & reflected wave phasor matrix $[V^-]$.

$$V_1^- = S_{11} V_1^+ + S_{12} V_2^+$$

$$V_2^- = S_{21} V_1^+ + S_{22} V_2^+$$

$$\text{or } \begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$\text{where } [V^-] = [S] [V^+] \quad [V^-] = \begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix}, [V^+] = \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

$$[S] = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}$$

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+=0} = \Gamma_{IN}$$

Input reflection coefficient when o/p port is terminated in a matched load

$$S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+=0}$$

Forward transmission coefficient when o/p port is terminated in a matched load

$$S_{12} = \left. \frac{V_1^-}{V_2^+} \right|_{V_1^+=0}$$

Reverse transmission coefficient when i/p port is terminated in a matched load

$$S_{22} = \left. \frac{V_2^-}{V_2^+} \right|_{V_1^+=0} = \Gamma_{OUT}$$

o/p reflection coefficient when i/p port is terminated in a matched load.

Properties of S-parameters

1) Reciprocal Networks. - A reciprocal N/w is defined as N/w that satisfies the reciprocity theorem.

For all reciprocal N/w's $[S]$ matrix is symmetrical.

$$\text{i.e. } S_{12} = S_{21}$$

2) A symmetrical reciprocal N/w's. - For all symmetrical reciprocal N/w's $[S]$ matrix is -

$$S_{11} = S_{22}$$

$$S_{12} = S_{21}$$

3) Lossless Networks

Unity property of S-matrix. - This property states that for a passive N/w lossless N-port N/w, the sum of the products of each term of any one row multiplied by its own complex conjugate is unity -

$$S_{11} \cdot S_{11}^* + S_{21} \cdot S_{21}^* = 1$$

$$S_{12} \cdot S_{12}^* + S_{22} \cdot S_{22}^* = 1$$

if lossless N/w is also reciprocal is $S_{12} = S_{21}$
 $S_{12} = S_{21}, |S_{11}| = |S_{22}|, |S_{11}|^2 + |S_{21}|^2 = 1$

Zero property of S-matrix - This property states that for a passive N/w the sum of products of each term of any row multiplied by complex conjugate of the corresponding terms of any other row is zero.

$$S_{11} \cdot S_{12}^* + S_{21} \cdot S_{22}^* = 0$$

$$S_{12} \cdot S_{11}^* + S_{22} \cdot S_{21}^* = 0$$

is lossless N/w is also reciprocal (i.e. $S_{12} = S_{21}$)


$$S_{12} = S_{21}$$

$$S_{11} \cdot S_{21}^* = S_{21} \cdot S_{22}^* = 0$$


$$|S_{11}| = |S_{22}|$$

Unit-II - Transmission Line Theory

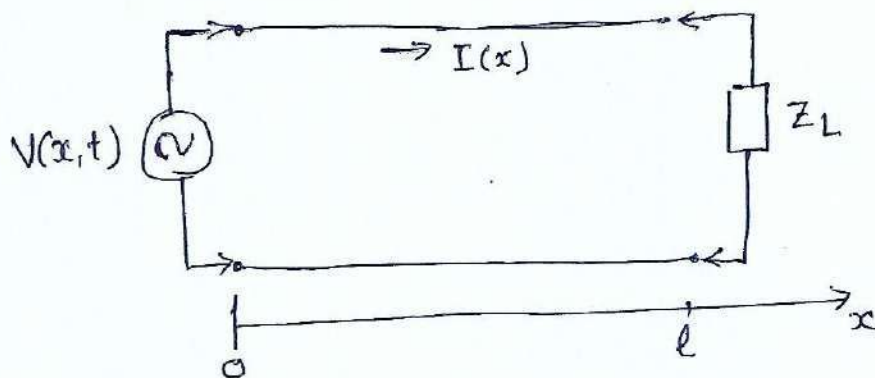
Let us consider two wires running parallel to each other having length l as shown below.



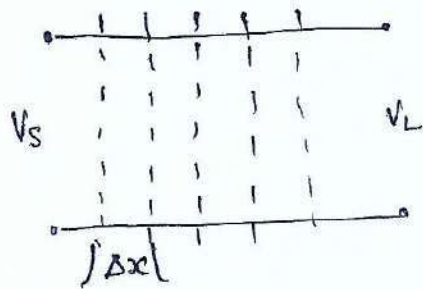
In order to find current $I(x)$ & voltage $V(x)$ at any point x , it is required to divide or make sub parts of Δx such that the wavelength λ should be comparable to length Δx of T.L. so that KVL & KCL can be applied to find $V(x)$ & $I(x)$




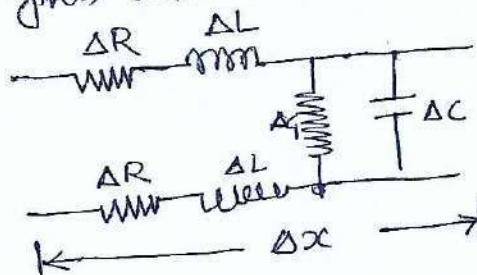Now the equivalent circuit of Δx can be drawn as given below:




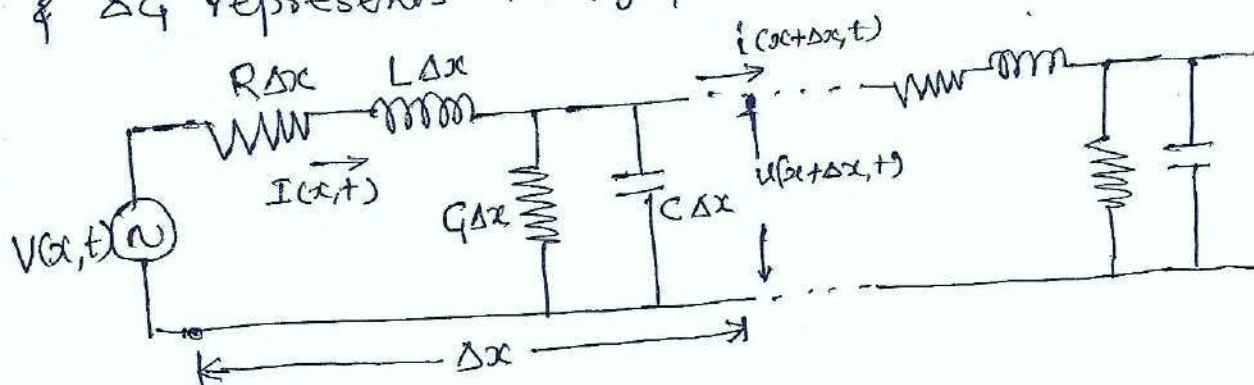ΔR represents skin resistance of wire, ΔL represents the self inductance of wire, ΔC represents capacitance between the two wires & ΔG represents leakage, which is represented by conductance.



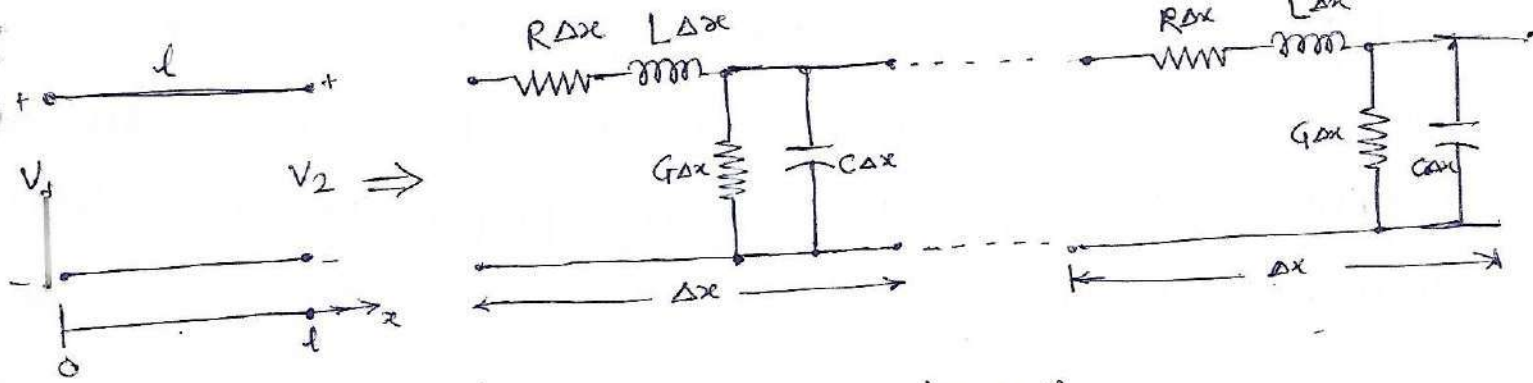

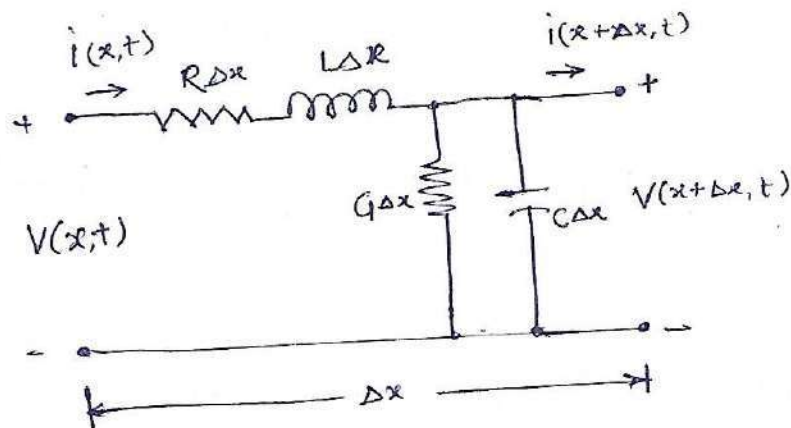As a thumb rule, when Ave. size of the discrete ckt component is more than a tenth of wavelength, the transmission line theory should be applied. $\lambda_A \gg \lambda/10$.



At high frequencies, a transmission line can be modeled as shown above.

To develop the governing differential equations, we will examine one Δx section of a transmission line as shown in Fig (b).

Using KVL for Δx section, we can write

$$V(x,t) = i(x,t) \cdot R\Delta x + L\Delta x \cdot \frac{\partial i(x,t)}{\partial t} + V(x+\Delta x,t) \quad (1)$$

Upon rearranging & dividing both sides by Δx , we obtain

$$-\frac{V(x+\Delta x,t) - V(x,t)}{\Delta x} = R \cdot i(x,t) + L \frac{\partial i(x,t)}{\partial t} \quad (2)$$

Letting $\Delta x \rightarrow 0$, gives

$$-\frac{\partial V(x,t)}{\partial x} = R \cdot i(x,t) + L \frac{\partial i(x,t)}{\partial t} \quad (3)$$

Similarly, using KCL we can write

$$i(x,t) = V(x+\Delta x,t) \cdot G\Delta x + C\Delta x \cdot \frac{\partial V(x+\Delta x,t)}{\partial t} + i(x+\Delta x,t) \quad (4)$$

Upon rearranging terms, dividing by Δx & letting $\Delta x \rightarrow 0$ gives.

$$-\frac{\partial i(x,t)}{\partial x} = G \cdot V(x,t) + C \frac{\partial V(x,t)}{\partial t} \quad (5)$$

Eqs. (3) & (5) are cross-coupled equations in terms of i & v .

These eqns can be separated by first differentiating both equations with respect to x & then properly substituting for terms, which leads to—

$$-\frac{\partial^2 V(x,t)}{\partial x^2} = R \cdot \frac{\partial i(x,t)}{\partial x} + L \frac{\partial^2 i(x,t)}{\partial x \partial t}$$

$$= -R \left[G \cdot V(x,t) + C \cdot \frac{\partial V(x,t)}{\partial t} \right] - L \left[G \frac{\partial V(x,t)}{\partial t} + C \cdot \frac{\partial^2 V(x,t)}{\partial t^2} \right]$$

or

$$\frac{\partial^2 V(x,t)}{\partial x^2} = LC \frac{\partial^2 V(x,t)}{\partial t^2} + (RC + LG) \cdot \frac{\partial V(x,t)}{\partial t} + RG \cdot V(x,t) \quad \text{--- (6)}$$

Similarly for i we can get,

$$\frac{\partial^2 i(x,t)}{\partial x^2} = LC \cdot \frac{\partial^2 i(x,t)}{\partial t^2} + (RC + LG) \cdot \frac{\partial i(x,t)}{\partial t} + RG i(x,t) \quad \text{--- (7)}$$

For sinusoidal signal variations for v & i , we can write corresponding phasors as follows.

$$V(x,t) = \operatorname{Re} [V(x) \cdot e^{j\omega t}]$$

$$I(x,t) = \operatorname{Re} [I(x) \cdot e^{j\omega t}]$$

Differentiating a time domain sinusoid $d(x(t))/dt$ amounts to the multiplication of the corresponding phasor (A) by $j\omega$.

Using this property eq. (6) & (7) can be written as—

$$\frac{d^2 V(x)}{dx^2} - p^2 V(x) = 0$$

$$\frac{d^2 I(x)}{dx^2} - p^2 I(x) = 0$$

$$\text{Where } p = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$