

$$V = V^+ e^{-\gamma x} + V^- e^{+\gamma x} \quad \& \quad I = \frac{V^+}{Z_0} e^{-\gamma x} - \frac{V^-}{Z_0} e^{+\gamma x}$$

$$\cosh \gamma x = \frac{e^{\gamma x} + e^{-\gamma x}}{2} \quad \sinh \gamma x = \frac{e^{\gamma x} - e^{-\gamma x}}{2}$$

$$\cosh \gamma x - \sinh \gamma x = \frac{1}{2} [e^{\gamma x} + e^{-\gamma x} - e^{\gamma x} + e^{-\gamma x}] = e^{-\gamma x}$$

$$\cosh \gamma x + \sinh \gamma x = e^{+\gamma x}$$

$$V = V^+ (\cosh \gamma x - \sinh \gamma x) + V^- (\cosh \gamma x + \sinh \gamma x)$$

$$V = \cosh \gamma x (V^+ + V^-) - \sinh \gamma x (V^+ - V^-)$$

$$\text{Similarly} \quad I = \frac{1}{Z_0} [\cosh \gamma x (V^+ - V^-) - \sinh \gamma x (V^+ + V^-)]$$

At input side i.e. at $x=0$ $V = V_s$ & $I = I_s$

$$\therefore \cosh \gamma x = 1 \quad \& \quad \sinh \gamma x = 0$$

$$V_s = V^+ + V^- \quad \& \quad I_s = \frac{V^+ - V^-}{Z_0}$$


$$V = V_s \cosh \gamma x - I_s Z_0 \sinh \gamma x$$

$$I = I_s \cosh \gamma x - \left(\frac{V_s}{Z_0} \right) \sinh \gamma x$$

$$Z_{in}(x) = Z_0 \cdot \frac{e^{-\gamma l} + \Gamma_L e^{+\gamma l}}{e^{-\gamma l} - \Gamma_L e^{+\gamma l}} \quad \text{where } \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$Z_{in}(x) = Z_0 \cdot \left[\frac{Z_L + Z_0 \tanh \gamma x}{Z_0 + Z_L \tanh \gamma x} \right]$$

OPEN-CIRCUITED T/L

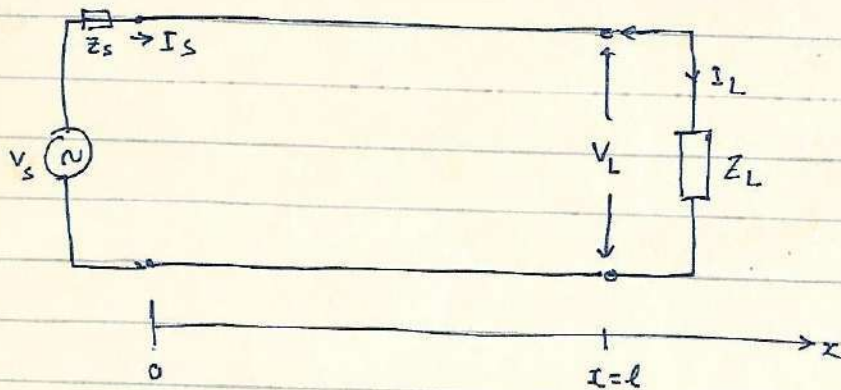

$$V_L = V_s \cosh \gamma l - I_s Z_0 \sinh \gamma l$$

$$I_L = I_s \cosh \gamma l - \frac{V_s}{Z_0} \sinh \gamma l$$

For open-circuited T/L, $I_L = 0$

$$0 = I_s \cosh \gamma l - \frac{V_s}{Z_0} \sinh \gamma l$$

$$Z_{oc} = \frac{V_s}{I_s} = Z_0 \frac{\cosh \gamma l}{\sinh \gamma l}$$

$$\boxed{Z_{oc} = Z_0 \coth \gamma l} \quad - (1)$$

For short-circuited T/L, $V_L = 0$

$$0 = V_s \cosh \gamma l - I_s Z_0 \sinh \gamma l$$

$$Z_{sc} = \frac{V_s}{I_s} = \frac{Z_0 \sinh \gamma l}{\cosh \gamma l}$$

$$\boxed{Z_{sc} = Z_0 \tanh \gamma l} \quad - (2)$$

Multiplying (1) & (2) $Z_{oc} \cdot Z_{sc} = Z_0 \coth \gamma l \cdot Z_0 \tanh \gamma l = Z_0^2$

$$\boxed{Z_0 = \sqrt{Z_{oc} \cdot Z_{sc}}}$$

Dividing (2) by (1)

$$\frac{Z_{sc}}{Z_{oc}} = \frac{Z_0 \tanh \gamma l}{Z_0 \coth \gamma l} = \tanh^2 \gamma l$$

$$\boxed{\tanh \gamma l = \sqrt{\frac{Z_{sc}}{Z_{oc}}}}$$

Open & Short Circuited Lossless Transmission Lines:

We have : $V_L = V_s \cosh \gamma l - I_s Z_0 \sinh \gamma l$

$$I_L = I_s \cosh \gamma l - \frac{V_s}{Z_0} \sinh \gamma l$$

For lossless: $\alpha = 0$

$$\gamma = \alpha + j\beta = j\beta$$

$$V_L = V_s \cosh j\beta l - I_s Z_0 \sinh j\beta l$$

$$\therefore \cosh j\beta l = \cos \beta l$$

$$\therefore V_L = V_s \cos \beta l - j I_s Z_0 \sin \beta l$$

$$\sinh j\beta l = j \sin \beta l$$

$$\& I_L = I_s \cos \beta l - j \frac{V_s}{Z_0} \sin \beta l$$

$$V_L = V_s \cos \beta l - j I_s Z_0 \sin \beta l$$

$$I_L = I_s \cos \beta l - j \frac{V_s}{Z_0} \sin \beta l$$


For Open-Circuited T/L: $I_L = 0$

$$0 = I_s \cos \beta l - j \frac{V_s}{Z_0} \sin \beta l$$

$$Z_{oc} = \frac{V_s}{I_s} = \frac{Z_0 \cos \beta l}{j \sin \beta l} \times \frac{j}{j}$$

$$Z_{oc} = -j Z_0 \cot \beta l$$
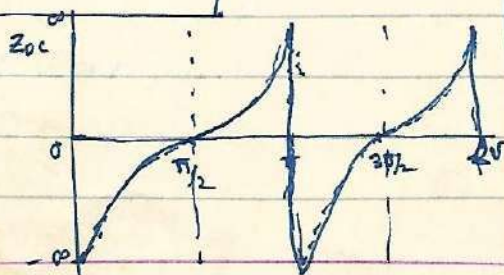
$$\begin{aligned} \beta &= \frac{2\pi l}{\lambda} \\ &= \frac{2\pi \cdot \frac{\lambda}{4}}{\lambda} \\ &= \frac{\pi}{2} \\ \beta &= \frac{2\pi \cdot \frac{\lambda}{2}}{\lambda} \end{aligned}$$



For short-Circuited T/L: $V_L = 0$

$$0 = V_s \cos \beta l - j I_L Z_0 \sin \beta l$$

$$Z_{sc} = \frac{V_s}{I_s} = j \frac{Z_0 \sin \beta l}{\cos \beta l}$$

$$Z_{sc} = j Z_0 \tan \beta l$$


$\lambda/2 - \lambda$
repeats for $\lambda/2$

$$l=0 \quad Z_{sc} = 0$$


$$0 \leq \beta l \leq \frac{\pi}{2} \quad Z_{sc} \text{ pu } \text{imp. } \uparrow$$

$$\text{at } l = \lambda/4 \Rightarrow Z_{sc} = \infty \text{ open}$$
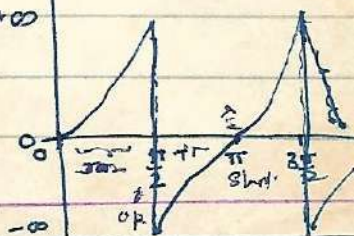
$$\frac{\lambda}{4} - \frac{\lambda}{2} \Rightarrow Z_{sc} = -j \text{ capac.}$$



OPEN-CIRCUITED T/L

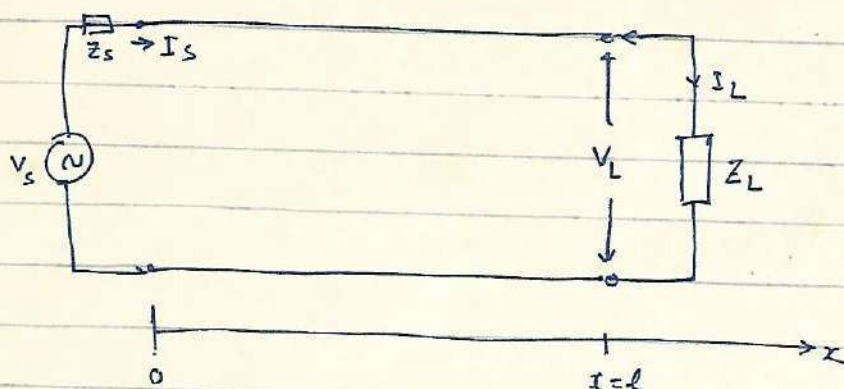

$$V_L = V_s \cosh \gamma l - I_s Z_0 \sinh \gamma l$$

$$I_L = I_s \cosh \gamma l - \frac{V_s}{Z_0} \sinh \gamma l$$

For open-circuited T/L, $I_L = 0$

$$0 = I_s \cosh \gamma l - \frac{V_s}{Z_0} \sinh \gamma l$$

$$Z_{oc} = \frac{V_s}{I_s} = Z_0 \frac{\cosh \gamma l}{\sinh \gamma l}$$

$$\boxed{Z_{oc} = Z_0 \coth \gamma l} \quad - (1)$$

For short-circuited T/L, $V_L = 0$

$$0 = V_s \cosh \gamma l - I_s Z_0 \sinh \gamma l$$

$$Z_{sc} = \frac{V_s}{I_s} = \frac{Z_0 \sinh \gamma l}{\cosh \gamma l}$$

$$\boxed{Z_{sc} = Z_0 \tanh \gamma l} \quad - (2)$$

Multiplying (1) & (2) $Z_{oc} \cdot Z_{sc} = Z_0 \coth \gamma l \cdot Z_0 \tanh \gamma l = Z_0^2$

$$\boxed{Z_0 = \sqrt{Z_{oc} \cdot Z_{sc}}}$$

Dividing (2) by (1)

$$\frac{Z_{sc}}{Z_{oc}} = \frac{Z_0 \tanh \gamma l}{Z_0 \coth \gamma l} = \tanh^2 \gamma l$$

$$\boxed{\tanh \gamma l = \sqrt{\frac{Z_{sc}}{Z_{oc}}}}$$

$$V(x) = V^+(x) + V^-(x)$$

$$V^+(x) = V_0^+ e^{-j\beta x} \quad V^-(x) = V_0^- e^{+j\beta x}$$

$$= V_0^+ e^{-j\beta x} + V_0^- e^{+j\beta x}$$

$$= V_0^+ (e^{-j\beta x} + \Gamma_L e^{+j\beta x})$$

$$\Gamma_L = \frac{V_0^-}{V_0^+}$$

$$V_0^- = \Gamma_L V_0^+$$

$$\Gamma = \frac{V_0^-}{V_0^+} e^{2j\beta x}$$

$$= \Gamma_L e^{2j\beta x}$$

$$I(x) = \frac{V_0^+}{Z_0} (e^{-j\beta x} - \Gamma_L e^{+j\beta x})$$

$$\therefore Z(x) = Z_0 \cdot \frac{e^{-j\beta x} + \Gamma_L e^{+j\beta x}}{e^{-j\beta x} - \Gamma_L e^{+j\beta x}}$$

$$Z(-l) = Z_0 \cdot \frac{e^{+j\beta l} + \Gamma_L e^{-j\beta l}}{e^{+j\beta l} - \Gamma_L e^{-j\beta l}}$$

$$\Gamma = \alpha + j\beta = j\beta$$

$$Z(-l) = Z_0 \cdot \frac{e^{+j\beta l} + \Gamma_L e^{-j\beta l}}{e^{+j\beta l} - \Gamma_L e^{-j\beta l}}$$

$$Z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right)$$

$$V(-l) = V_0^+ [e^{+j\beta l} + \Gamma_L e^{-j\beta l}]$$

$$I(-l) = \frac{V_0^+}{Z_0} [e^{+j\beta l} - \Gamma_L e^{-j\beta l}]$$

$$Z_{in} = Z_0 \left(\frac{Z_L + Z_0 \tanh \beta l}{Z_0 + Z_L \tanh \beta l} \right)$$

$$\begin{aligned} e^{+j\beta l} &= \cos \beta l + j \sin \beta l \\ e^{-j\beta l} &= \cos \beta l - j \sin \beta l \end{aligned} \quad \text{Euler's Eqn.}$$

$$Z_{in} = Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right)$$

Special cases.

$$l = \frac{\lambda}{2}, \quad \beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} = \pi$$

$$\cos \beta l = \cos \pi = -1 \quad \& \quad \sin \beta l = 0$$

$$\therefore Z_{in} = Z_L \quad \text{independent of } Z_0 \text{ or } \beta$$

$$(2) \quad l = \frac{\lambda}{4}, \quad \beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2}$$

$$\cos \beta l = \cos \frac{\pi}{2} = 0 \quad \& \quad \sin \beta l = 1$$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

$Z_L = 0$ short
 $Z_{in} = \infty$ open
& vice-versa.

$$(3) \quad Z_L = jX_L \quad \text{Load is purely Reactive.}$$

$$Z_{in} = Z_0 \left(\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right)$$

$$= Z_0 \left(\frac{jX_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j^2 X_L \sin \beta l} \right)$$

$$= Z_0 \left(\frac{X_L \cos \beta l + Z_0 \sin \beta l}{Z_0 \cos \beta l - X_L \sin \beta l} \right)$$

If transmission line is electrically small, its length l is small wrt to signal wavelength λ

$$(4) \quad l \ll \lambda$$

$$\beta l = \frac{2\pi}{\lambda} l \approx 2\pi \cdot \frac{l}{\lambda} \approx 0$$

$$\cos \beta l = \cos 0 = 1$$

$$\& \quad \sin \beta l = \sin 0 = 0$$

$$\left. \begin{aligned} V(-l) &= V(0) \\ I(-l) &= I(0) \end{aligned} \right\} \text{if } l \ll \lambda$$

$$V(-l) = V_0^+ + \Gamma_L V_0^+$$

$$V(0) =$$

$$Z_{in} = Z_L$$

$$(3) \quad \text{if } Z_L = Z_0$$

$$Z_{in} = Z_0$$

i.e. if load imp. is equal to Z_0 then i/p imp of T.L. will also be Z_0 regardless of length of transmission line.

If load is purely reactive then, input impedance will also be purely reactive.

Impedance Matching

- i) Quarter Wave transformer (Impedance Inverter)
- ii) stub matching.

$$Z_{in} = Z_0 \frac{e^{+j\beta l} + \Gamma_L e^{-j\beta l}}{e^{+j\beta l} - \Gamma_L e^{-j\beta l}}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\cosh px = \frac{e^{+px} + e^{-px}}{2}, \quad \sinh px = \frac{e^{+px} - e^{-px}}{2}$$

$$\therefore Z_{in} = Z_0 \cdot \frac{Z_L + Z_0 \tanh \beta l}{Z_0 + Z_L \tanh \beta l}$$

if $Z_L = 0$ short

$$Z_{in} = Z_0 \tanh \beta l = j Z_0 \tan \beta l$$

for lossless xml line $\beta = j\beta$

$$\tanh j\beta l = j \tan \beta l, \quad \sinh j\beta l = j \sin \beta l, \quad \cosh j\beta l = \cos \beta l$$

$$\tan j\beta l = \frac{\sinh j\beta l}{\cosh j\beta l} = j \frac{\sin \beta l}{\cos \beta l} = j \tan \beta l$$

$$Z_{in} = Z_0 \cdot \left[\frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right]$$

$$\text{If } l = \frac{\lambda}{4}, \quad \beta = \frac{2\pi}{\lambda}$$

$$\beta l = \text{electrical length} = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \pi/2$$

$$Z_s = Z_0 \left[\frac{Z_L + j Z_0 \tan \pi/2}{Z_0 + j Z_L \tan \pi/2} \right]$$

$$\sin \pi/2 = 1$$

$$\cos \pi/2 = 0$$

$$\therefore \tan \pi/2 = \frac{1}{0} = \infty$$

$$= Z_0 \left[\frac{Z_L \cos \pi/2 + j Z_0 \sin \pi/2}{Z_0 \cos \pi/2 + j Z_L \sin \pi/2} \right]$$

$$= Z_0 \left[\frac{Z_L \cdot 0 + j Z_0 \cdot 1}{Z_0 \cdot 0 + j Z_L \cdot 1} \right]$$

$$= Z_0 \left[\frac{j Z_0}{j Z_L} \right] = \frac{Z_0^2}{Z_L}$$

$$\boxed{Z_s = \frac{Z_0^2}{Z_L}}$$

$$Z_s \propto \frac{1}{Z_L}$$

Input imp is inversely proportional to load imp

if $Z_s \downarrow$, $Z_L \uparrow$ vice-versa.

if Z_0 is resistive

if Z_L is Capacitive $\rightarrow Z_s$ inductive & vice-versa.

$\lambda/4$ line acts as step-up or step down impedance transformer