

But $\cos^{-1}(-|\Gamma_L|) = \cos^{-1}|\Gamma_L| - \pi$ — (3)

hence $\phi - 2\beta l_s = \cos^{-1}|\Gamma_L| - \pi$ — (3)

$$2\beta l_s = \phi + \pi - \cos^{-1}|\Gamma_L|$$

$$l_s = \frac{\phi + \pi - \cos^{-1}|\Gamma_L|}{2\beta}$$

$$\boxed{l_s = \frac{\lambda}{4\pi} [\phi + \pi - \cos^{-1}|\Gamma_L|]}$$

Again from eq. (3) the shunt susceptance —

$$\frac{B_s}{G_0} = \frac{-2|\Gamma_L| \sin \phi'}{1 + |\Gamma_L|^2 + 2|\Gamma_L| \cos \phi'} = \frac{-2|\Gamma_L| \sin(\phi - 2\beta l_s)}{1 + |\Gamma_L|^2 + 2|\Gamma_L| \cos(\phi - 2\beta l_s)} \quad (4)$$

Put eq. (3) in eq (4)

$$\frac{B_s}{G_0} = \frac{-2|\Gamma_L| \sin[\cos^{-1}|\Gamma_L| - \pi]}{1 + |\Gamma_L|^2 + 2|\Gamma_L|(-|\Gamma_L|)}$$

$$\boxed{\frac{B_s}{G_0} = \frac{-2|\Gamma_L| \sin[\cos^{-1}|\Gamma_L|]}{1 + |\Gamma_L|^2 - 2|\Gamma_L|^2}} \quad (5)$$

In order to find $\sin\{\cos^{-1}|\Gamma_L|\}$, let us put $\cos^{-1}|\Gamma_L| = \theta$

$$\therefore |\Gamma_L| = \cos \theta$$

$$\sin \theta = \sqrt{1 - \cos^2 \theta} = \sqrt{1 - |\Gamma_L|^2}$$

$$\therefore \text{eq (5)} \quad \frac{B_s}{G_0} = \frac{-2|\Gamma_L| \sin \theta}{1 + |\Gamma_L|^2 - 2|\Gamma_L|^2} = \frac{-2|\Gamma_L| \cdot \sqrt{1 - |\Gamma_L|^2}}{1 - |\Gamma_L|^2}$$

$$\boxed{B_s = G_0 \left[\frac{-2|\Gamma_L|}{\sqrt{1 - |\Gamma_L|^2}} \right]} \quad (c)$$

Now if B_s is Susceptance of stub & B_L line sus.
 then in order to cancel the Susceptance, both
 must be Zero at point of attachment.

$$\therefore B_s + B_L = 0$$

$$B_L = -B_s = -\left[G_0 \frac{\{2|\Gamma_L|\}}{\sqrt{1-|\Gamma_L|^2}}\right]$$

$$\text{OR } B_L = G_0 \left[\frac{2|\Gamma_L|}{\sqrt{1-|\Gamma_L|^2}} \right]$$

But Susceptance of short-circuited stub is -

$$B_L = G_0 \cot \beta l_t$$


l_t = length of short
 circuited stub.

$$G_0 \cot \beta l_t = G_0 \left\{ \frac{2|\Gamma_L|}{\sqrt{1-|\Gamma_L|^2}} \right\}$$

$$\frac{1}{\tan \beta l_t} = \frac{2|\Gamma_L|}{\sqrt{1-|\Gamma_L|^2}} \quad \text{or } \tan \beta l_t = \frac{\sqrt{1-|\Gamma_L|^2}}{2|\Gamma_L|}$$

$$\beta l_t = \tan^{-1} \frac{\sqrt{1-|\Gamma_L|^2}}{2|\Gamma_L|}$$

$$\therefore \boxed{l_t = \frac{\lambda}{2\pi} \tan^{-1} \frac{\sqrt{1-|\Gamma_L|^2}}{2|\Gamma_L|}} \quad \text{--- (B)}$$

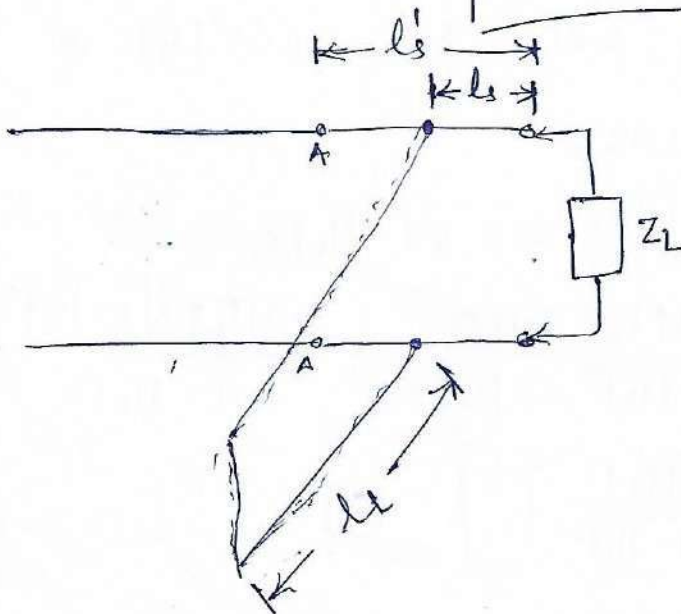

(5)

From eq (A): $\frac{G_s}{G_0} = \frac{1 - |\Gamma_L|^2}{1 + |\Gamma_L|^2 + 2|\Gamma_L| \cos(\phi - 2\beta l_s)}$

This value of $\frac{G_s}{G_0}$ is maximum when denominator is minimum

i.e. When $\cos(\phi - 2\beta l_s) = -1$

Thus cosine term should be -1 for maximum value of $l_s = l'_s$

$$\cos(\phi - 2\beta l'_s) = -1$$

$$\phi - 2\beta l'_s = \cos^{-1}(-1) = \pi$$

$$\text{or } \phi = 2\beta l'_s = \pi$$

$$l'_s = \frac{\phi + \pi}{2\beta} = \frac{\phi + \pi}{2 \times \frac{2\pi}{\lambda}} = \frac{\lambda(\phi + \pi)}{4\pi}$$

$$\boxed{l'_s = \frac{\lambda(\phi + \pi)}{4\pi}}$$

$\therefore$ At a distance l'_s from load the value of

$$\begin{aligned} \frac{G_s}{G_0} &= \frac{1 - |\Gamma_L|^2}{1 + |\Gamma_L|^2 + 2|\Gamma_L|(-1)} = \frac{(1 - |\Gamma_L|)(1 + |\Gamma_L|)}{(1 - |\Gamma_L|)^2} \\ &= \frac{(1 - |\Gamma_L|)(1 + |\Gamma_L|)}{(1 - |\Gamma_L|)(1 - |\Gamma_L|)} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \text{VSWR} = S \end{aligned}$$

$$\frac{G_s}{G_0} = S$$

$$\text{But } G_s = \frac{1}{Z_s} = \frac{1}{R_s}$$

$$G_0 = \frac{1}{Z_0} = \frac{1}{R_0}$$

$$\frac{1}{Z_s} \cdot Z_0 = S$$

$$\boxed{Z_s = \frac{Z_0}{S}}$$

This is the point of maximum $\frac{G_s}{G_0}$ which is recognized as a point of minimum voltage at a distance of l'_s from load.

At a distance l_s from load, the value of $\frac{G_s}{G_0} = 1$ or $G_s = G_0$. This

is the point where stub is attached.

Value of distance d is given by

$$d = l'_s - l_s = \frac{\phi + \pi}{2\beta} - \frac{\phi + \pi - \cos^{-1}|\Gamma_L|}{2\beta}$$

$$d = \frac{\cos^{-1}|\Gamma_L|}{2\beta}$$

$$\boxed{d = \frac{\lambda}{4\pi} \cos^{-1} \left(\frac{VSWR-1}{VSWR+1} \right)}$$

This shows that stub should be connected at distance d measured in either direction from voltage minimum point A . Normally stub is attached towards load side of that minimum which is nearest to the load voltage standing wave ratio which is existing before the attachment of stub.

$$l_t = \frac{\lambda}{2\pi} \tan^{-1} \frac{\sqrt{1-|\Gamma_L|^2}}{2|\Gamma_L|}$$

$$\text{But } |\Gamma_L| = \frac{VSWR-1}{VSWR+1} = \frac{S-1}{S+1}$$

$$\text{Putting } l_t = \frac{\lambda}{2\pi} \tan^{-1} \frac{\sqrt{1 - \left| \frac{S-1}{S+1} \right|^2}}{2 \left| \frac{S-1}{S+1} \right|}$$

$$\boxed{l_t = \frac{\lambda}{4\pi} \tan^{-1} \frac{\sqrt{S}}{S-1}} \text{ meter.}$$

If Z_0 is purely resistive $Z_0 = R_0$

Lossless line: $R=0$, $G=0$

$$\therefore Z_0|_{\text{lossless}} = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{\frac{L}{C}}$$

$$\boxed{Z_0 = \sqrt{\frac{L}{C}}}_{\text{lossless}}$$

For Distortionless: $RC = L G$

$$\text{or } \frac{R}{G} = \frac{L}{C} \quad \text{or } \frac{L}{R} = \frac{C}{G}$$

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{\frac{R}{G} \left(\frac{1+j\omega L/R}{1+j\omega C/G} \right)} = \sqrt{\frac{R}{G}}$$

$$\boxed{Z_0|_{\text{distortionless}} = \sqrt{\frac{L}{C}}}$$

$\therefore$ A lossless line is distortionless but a distortionless line is not always lossless.

Smith-Chart

We know the relation between reflection coefficient & impedance Z of a transmission line as:

$$\Gamma = \frac{Z - Z_0}{Z + Z_0} \quad \text{--- (1)}$$

Normalizing eq. (1) w.r.t. Z_0

$$\Gamma = \frac{Z_N - 1}{Z_N + 1}$$

where $Z_N = \frac{Z}{Z_0} = r + jx$.

Where Γ = reflection coefficient

Z = impedance at any point

Z_0 = Chara. impedance of T.L.

Thus Smith-chart is a plot of reflection coefficient versus normalized impedance of T.L. in T-plane as a function of r & x .

$$\Gamma = \frac{Z_N - 1}{Z_N + 1}$$

$$Z_N = r + jx$$

$$\Gamma = \frac{r + jx - 1}{r + jx + 1} = U + jV$$

Separating into real & imaginary parts.

$$U = \frac{r^2 - 1 + x^2}{(r+1)^2 + x^2} \quad \text{--- (2)}$$

$$V = \frac{2x}{(r+1)^2 + x^2} \quad \text{--- (3)}$$

Eqs (2) & (3), we can obtain two families of circles, that when superimposed on each other, will make up the entire Smith Chart.

1. Constant- r Circles - Eliminating x from eq. (2) & (3) gives

0) $r=0$, $C = (0, 0)$
 $R = 1$

1) $r=1$, $C = (0.5, 0)$
 $R = 0.5$

2) $r=2$, $C = (2/3, 0)$
 $R = 1/3$

3) $r=\infty$, $C = (1, 0)$

$$\left(U - \frac{r}{r+1}\right)^2 + V^2 = \left(\frac{1}{r+1}\right)^2 \quad \text{--- (4)}$$

Eq (4) is eqn. of circle with center located at $(U_0, V_0) = \left(\frac{r}{r+1}, 0\right)$

& radius $R = \left(\frac{1}{r+1}\right)$