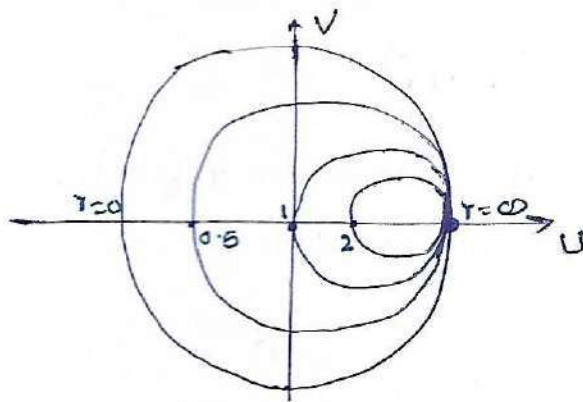




Constant r -circles.

2. Constant x -circles - Eliminating r from eq. (2) & (3) gives

$$(U-1)^2 + (V - \frac{1}{x})^2 = (\frac{1}{x})^2 \quad \text{--- (5)}$$

Eq. (5) represents constant x -circles with center located at $(U_0, V_0) = (1, \frac{1}{x})$

1) $x=0$

$C = (1, \infty)$

$r = \infty$

& radius $R' = \frac{1}{|x|}$

2) $x=1$

$C = (1, 1)$

$r = 1$

3) $x=2$


$C = (1, 0.5)$

$r = \frac{1}{2} = 0.5$


4) $x=\infty$

$C = (1, 0)$

$r = 0$

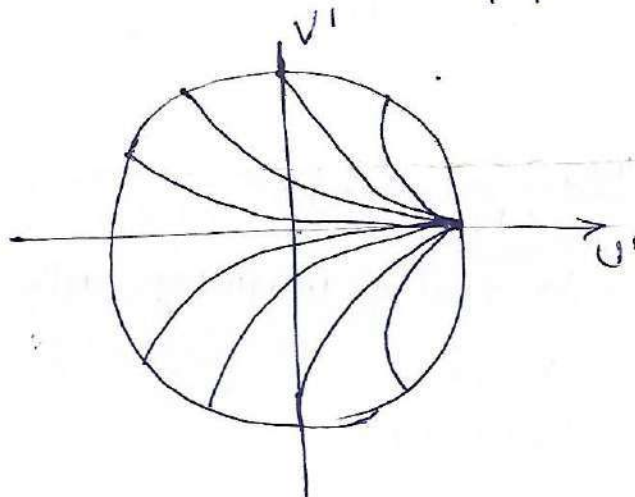

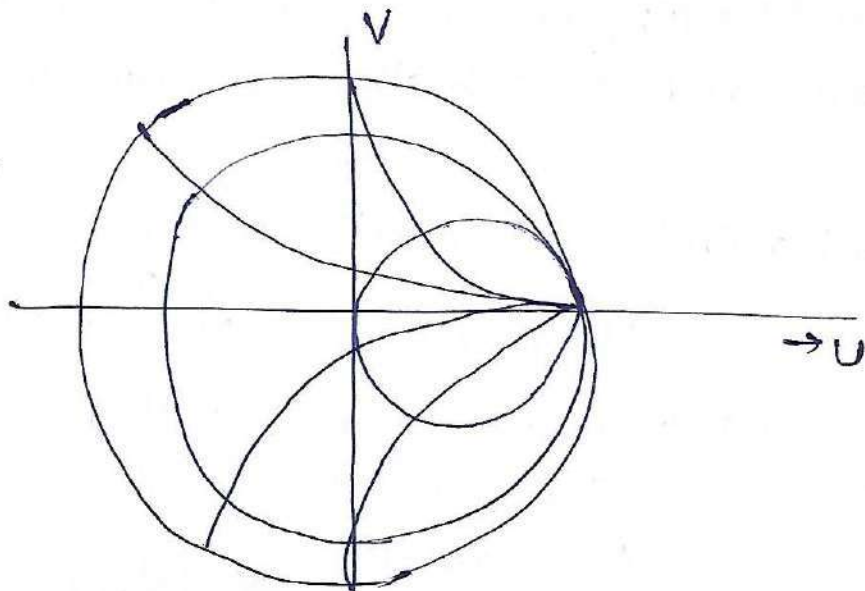When Circles r & x obtained in eq. (4) & (5) are superimposed it results into Smith-chart shown below.




Constant x -Circles

Now eliminating r from eq. ① & ②.

$$(U-1)^2 + (V - \frac{1}{x})^2 = (\frac{1}{x})^2$$

$$(U_0', V_0') = (1, \frac{1}{x})$$

$$R = \frac{1}{|x|}$$

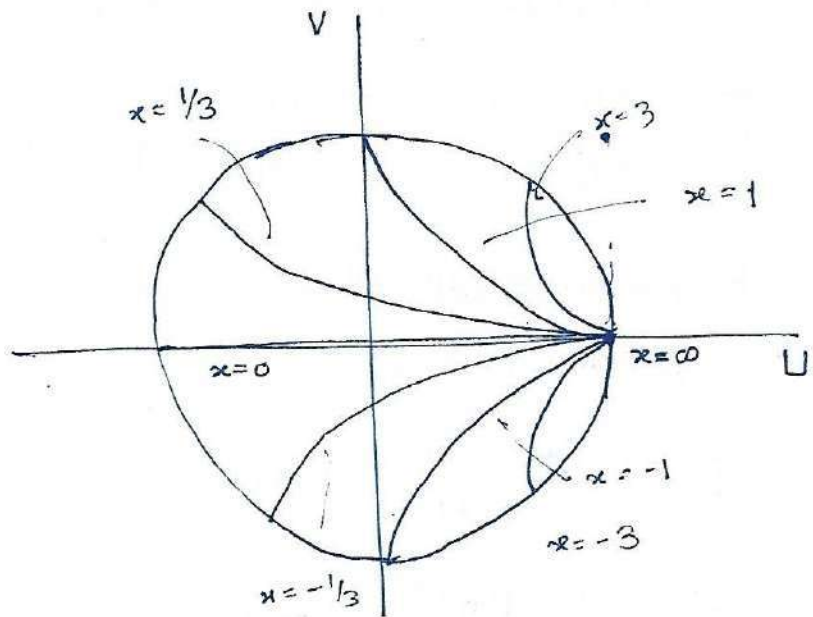


1) for $x = \infty$
 $U_0', V_0' = (1, 0)$
 $R = \frac{1}{\infty} = 0$

2) for $x = 0$
 $U_0', V_0' = (1, \infty)$
 $R = \infty$


3) $x = 1$, $U_0', V_0' = (1, 1)$
 $R = 1$

4) for $x = -1$
 $U_0', V_0' = (1, -1)$

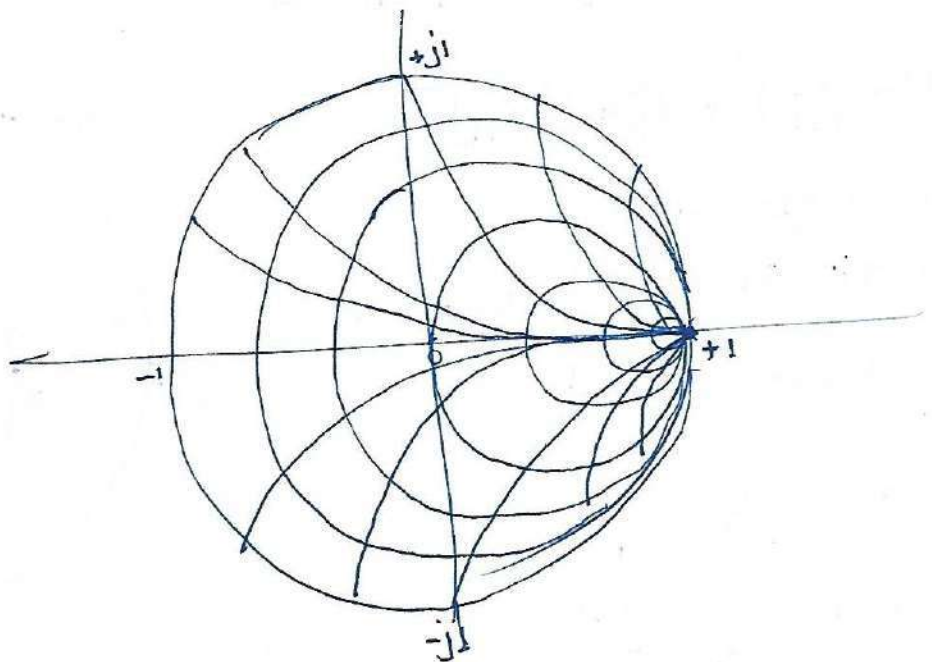

The Complete Smith Chart

Black Magic Design

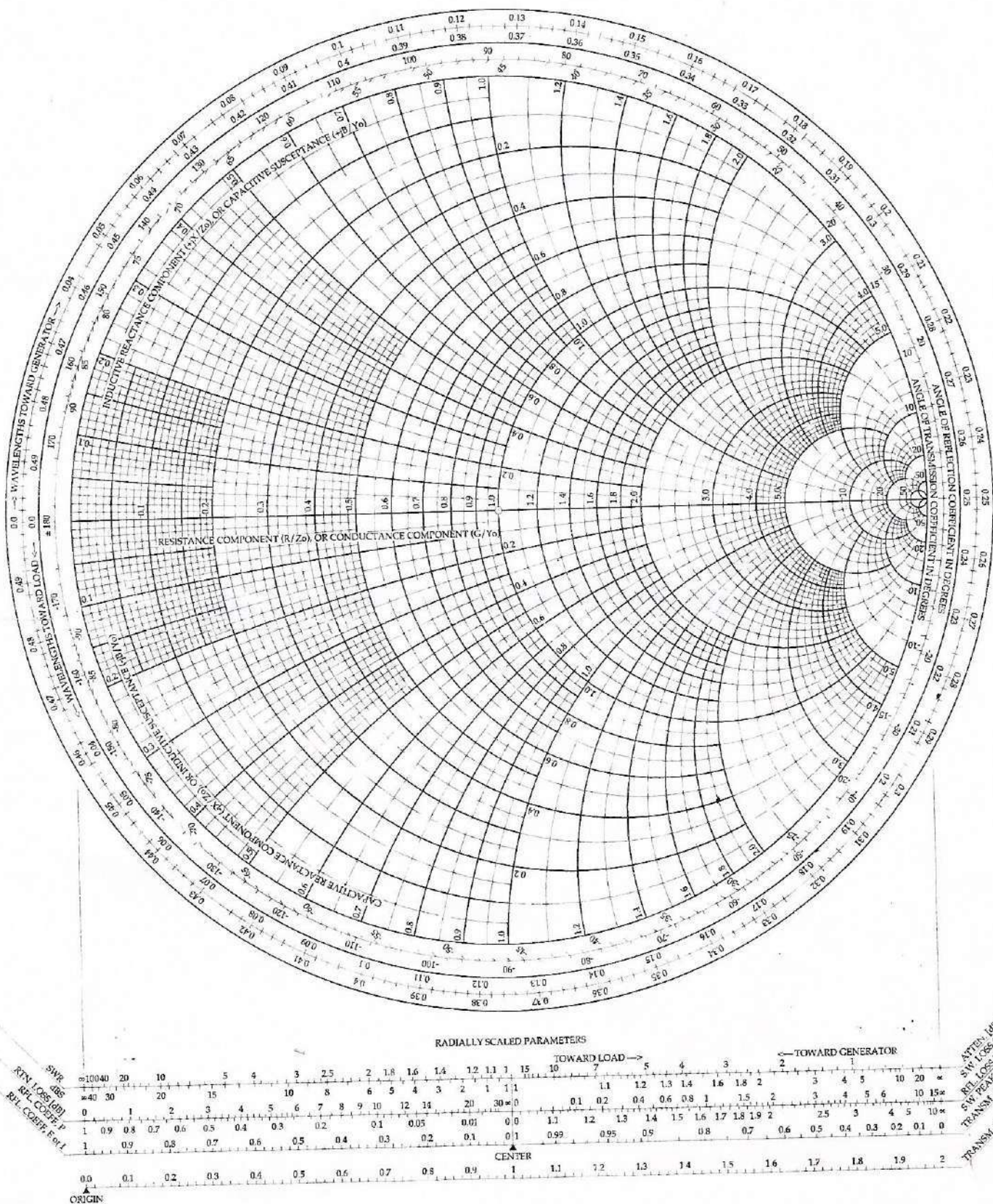

Input Impedance (Z_{IN}) if Z_L is known.


1. Plot normalized load impedance $(Z_L)_N = Z_L/Z_0$ on Smith chart
2. Draw the constant VSWR circle that goes thr. $(Z_L)_N$
3. Starting from $(Z_L)_N$, move 'towards generator' on constant VSWR circle a distance l/λ .
4. Read off the normalized i/p impedance value (Z_{IN}/Z_0) from chart.

1. Find the input impedance of a transmission line $Z_0 = 50 \Omega$ that has a length of $\lambda/8$ & is connected to a load impedance $Z_L = (50 + j50) \Omega$

Solⁿ - locate $(Z_L)_N = Z_L/Z_0 = 1 + j1$ on the Smith chart.

- Draw constant VSWR circle.
- Move 'towards gen' on constant VSWR circle a dis. $\lambda/8$
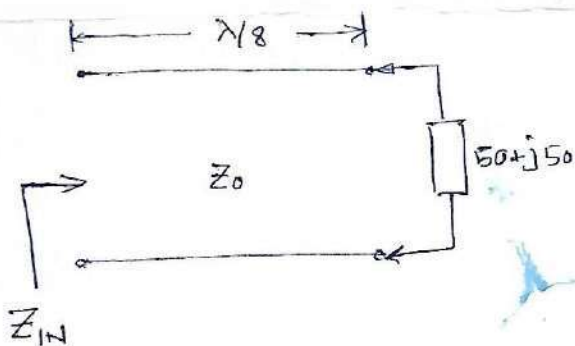
$$(Z_{IN})_N = 2 - j1 \quad Z_{IN} = Z_0 \cdot (Z_{IN})_N = (100 - j50) \Omega$$



$$Z_{IN} = Z_0 \cdot \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}$$

$$\beta = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{8} = \frac{\pi}{4}$$

— Input Impedance using r/p ref. Coefficient $|\Gamma_{IN}| \leq 1$

Locate $\Gamma_{IN} = |\Gamma_{IN}|e^{j\theta}$ on Smith Chart, the mag. of $|\Gamma|$ can be read off the ref. coeff. vol. radial scale at bottom of the chart while θ is read off the circular scale.

— Normalized values of resistance & reactance (r, x) can be read off the Smith chart at p.i.A.

$$Z_{IN} = Z_0 (r + jx)$$

① Calculate Z_0 , β , v_p at 400kc/s for T.L. having $L = 0.5\text{mH/km}$, $C = 0.08\text{uF/km}$ negligible R & G

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{0.5 \times 10^{-3}}{0.08 \times 10^{-6}}} = 79.08 \Omega$$

$$\beta = j\beta \quad \beta = j\omega\sqrt{LC} = j\beta$$

$$\beta = \omega\sqrt{LC} = j2\pi \times 400 \times 10^3 \sqrt{0.5 \times 10^{-3} \times 0.08 \times 10^{-6}}$$

$$= j15.9 \text{ per km}$$

$$|\beta| = 15.9 \text{ rad/km.}$$

$$V_p = \frac{\omega}{\beta} = \frac{\omega}{\omega\sqrt{LC}} = \frac{1}{\sqrt{0.5 \times 10^{-3} \times 0.08 \times 10^{-6}}}$$

$$= 1.58 \times 10^5 \text{ km/sec.}$$

② A lossless T.L. of 100Ω char. Imp. is connected to a load of 200Ω . Calculate voltage Ref. Coeff. & SWR.

$$Z_0 = 100\Omega$$

$$Z_L = 200\Omega$$

$$\Gamma = ?$$

$$\text{VSWR} = ?$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{200 - 100}{200 + 100} = \frac{1}{3}$$

$$\text{VSWR} = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 1/3}{1 - 1/3} = \frac{4}{2} = 2$$

③ A T.L. has following constants $R = 10.4\Omega$, $L = 3.66\text{mH}$, $C = 0.00835\text{uF}$, $G = 0.08\text{uS}$. Calculate Z_0 , α , β & v_p at $\omega = 5000 \text{ rad/sec}$.

$$\underline{\text{Sol}} \quad Z = R + j\omega L = 10.4 + j18.33 = 21.05 \angle 60.4^\circ$$

$$Y = G + j\omega C = 0.08 \times 10^{-6} + j41.75 \times 10^{-6} = 41.77 \times 10^{-6} \angle 89.9^\circ$$

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{21.05 \angle 60.4^\circ}{41.77 \times 10^{-6} \angle 89.9^\circ}} = 224.5 \angle -14.5^\circ$$

$$\rho = \sqrt{ZY} = 0.007561 + j0.02863$$

$$V_p = \frac{\omega}{\beta} = \frac{5000}{0.02863} = 1.746 \times 10^5 \text{ km/sec.}$$

- ④ A T.L. of Chara. imp. 600Ω is terminated by a reactance of $j150\Omega$, find input^{imp.} seen 25cm long at freq. of 300MHz .

Solⁿ $Z_0 = 600\Omega$, $Z_L = j150\Omega$
 $l = 25\text{cm} = \frac{25}{100} = \frac{1}{4}\text{m}$, $f = 300\text{MHz}$

$$\lambda = \frac{300}{300} = \lambda = 1\text{m}$$

$$\beta l = \frac{2\pi}{\lambda} \cdot \frac{1}{4} = \frac{2\pi}{1} \cdot \frac{1}{4} = \pi/2$$

$$Z_{in} = Z_0 \left[\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right]$$

$$= Z_0 \cdot \frac{Z_0^2}{Z_L} = \frac{600 \times 600}{j150} = \frac{j}{j}$$

$$Z_{in} = -j2400\Omega$$

- ⑤ A 50Ω lossless T.L. has pure reactance of $j100\Omega$ as its load. Find VSWR in the line.

Solⁿ. $Z_0 = 50\Omega$, $Z_L = j100\Omega$
 $\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{j100 - 50}{j100 + 50} = \frac{j2-1}{j2+1}$

$$|\Gamma_L| = \sqrt{\frac{4+1}{4+1}} = \sqrt{\frac{5}{5}} = 1$$

$$\text{VSWR} = \frac{1+|\Gamma_L|}{1-|\Gamma_L|} = \frac{1+1}{1-1} = \frac{2}{0} = \infty$$

- ⑥ A lossless T.L. having 50Ω Chara. imp. & length $\lambda/4$ is short circuited at one end & connected to an ideal volt. Source of 1V at other end. The current drawn from volt source is — $Z_0 = 50\Omega$, $l = \lambda/4$, $V_s = 1\text{V}$, $Z_L = 0\Omega$ (s.c.)

$$I_s = \frac{V_s}{Z_{in}}$$

For lossless $\lambda/4$ line $Z_{in} = \frac{Z_0^2}{Z_L} = \frac{50^2}{0} = \infty$

$$I_s = \frac{1}{\infty} = 0\text{A}$$