
 
 
 


Latch up in CMOS

Unit-5

 - Generation of low impedance path in CMOS circuit b/w V_{DD} (supply) & ground.
- so, high current will get driven by V_{DD} towards ground & that may damage in CMOS circuit



* forward bias

Anode - V_{DD}

cathode - ground



* gate pulse

SCR - turned on

- current will flow from V_{DD} to gnd. even though remove gate pulse
- ↳ latch-up of SCR
- same as in CMOS

  
Example of inverter using CMOS

$\frac{p}{n}$ substrate contact for PMOS & NMOS



equivalent ckt

multi emitter terminal

 

for latch in CMOS conditions:

① if V_{in} or $V_{out} > V_{DD}$

Q_1 - on

EB - forward Q_1

BE - forward Q_2

then current will flow from V_{DD} to ground.

② if V_{in} or $V_{out} < \text{ground}$

Q_2 - EB - forward - ON

Q_1 - BE - forward - ON

regenerative feedback

classmate

Date _____

Page _____

→ retrograde well
→ P on P⁺

Prevent latch-up steps

1. Add gold impurities in substrate, will minimize life time of minorities in transistor, that will reduce latch up.
2. By providing epitaxial layer, can reduce (R_{sub}) substrate resistance.
3. Substrate N-well as close placement of substrate & well as close as possible.
4. Avoid forward biasing of source & drain.
5. Place P-MOS close to V_{DD} & n-MOS close to ground.