

Binary Code converter circuit

Code converter circuits are designed to translate data representation from one format to another.


Binary-to-Gray code converter takes binary input & translates it to the corresponding output.

Gray code is an ordering of the binary numeral system such that two successive values differ in only one bit.

BINARY to GRAY

- The most significant bit of Binary & Gray are always equal.

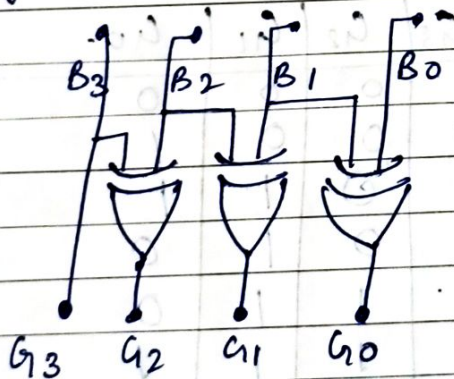- Other bits of the output gray code can be XORed with the adjacent bit.



Binary to Gray
code converter
circuit.

Gray to Binary Conversion


- The MSB of Binary is always equal to Gray Code.


- If G_3 is MSB $\rightarrow G_3 \ G_2 \ G_1 \ G_0$
the output variables $\rightarrow B_3 = G_3$

$$B_2 = G_2 \oplus G_3$$

$$B_1 = G_1 \oplus G_2 \oplus G_3$$
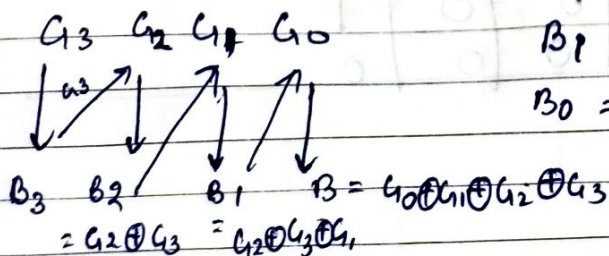
$$B_0 = G_0 \oplus G_1 \oplus G_2 \oplus G_3$$



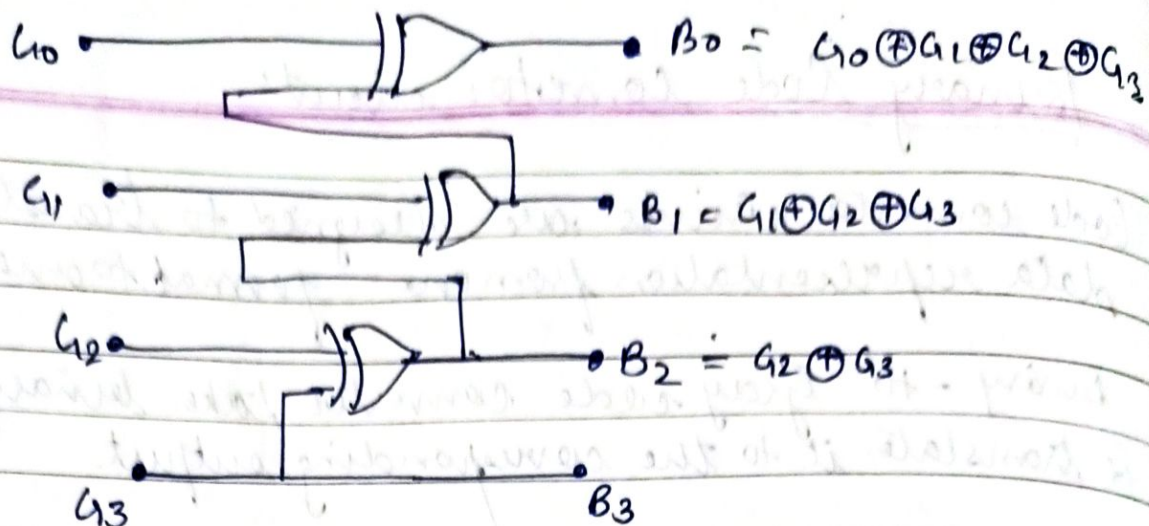

Eg. $\rightarrow$ Binary $\begin{matrix} \oplus & \oplus & \oplus & \oplus & \oplus \\ 1 & 0 & 0 & 1 & 1 \end{matrix}$
 $\downarrow$
 Gray $\downarrow$
 Gray $\rightarrow 1\ 0\ 1\ 0\ 1\ 0$
 $\swarrow \nearrow \nearrow \nearrow \nearrow$
 Binary $\downarrow \nearrow \nearrow \nearrow \nearrow$
 $1\ 1\ 0\ 0\ 1\ 1$

4 Bit Binary to Gray Code Truth Table

B_3	B_2	B_1	B_0	G_3	G_2	G_1	G_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

BCD To Excess 3 Code Converter

- The process of converting BCD to excess 3 is quite simpler than other conversion. It is done by calculating by adding 3 (0011) to each four bit BCD code.

For eg. BCD for 8 $\rightarrow$ 1000
 and 3 $\rightarrow$ 1000 + 0011

$$\begin{array}{r} 1000 \\ + 0011 \\ \hline 1011 \end{array}$$

Tenth Table for Bcd to Excess-3.

A B C D					W	X	Y	Z
Decimal	B	C	D	Code	Excess - 3			
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	0	X	X	X	X
11	1	0	1	1	X	X	X	X
12	1	1	0	0	X	X	X	X
13	1	1	0	1	X	X	X	X
14	1	1	1	0	X	X	X	X
15	1	1	1	1	X	X	X	X

Decimal

We make K Map to draw circuit

K Map for w

CD \ AB	AB			
	00	01	11	10
00	0	4	X ₁₂	8
01	1	5	X ₁₃	9
11	3	7	X ₁₅	X ₁₁
10	2	6	X ₁₄	X ₁₀

$$W = A + BC + BD$$

K Map for X

CD \ AB	AB			
	00	01	11	10
00	0	4	X ₁₂	8
01	1	5	X ₁₃	9
11	3	7	X ₁₅	X ₁₁
10	2	6	X ₁₄	X ₁₀

$$X = B'C + B'D + B'C'D$$

K Map for Y


CD \ AB	AB			
	00	01	11	10
00	1	4	X ₁₂	8
01	1	5	X ₁₃	9
11	3	7	X ₁₅	X ₁₁
10	2	6	X ₁₄	X ₁₀

$$Y = C'D + CD$$

K Map for Z

CD \ AB	AB			
	00	01	11	10
00	1	4	X ₁₂	8
01	1	5	X ₁₃	9
11	3	7	X ₁₅	X ₁₁
10	2	6	X ₁₄	X ₁₀

$$Z = \overline{D}$$

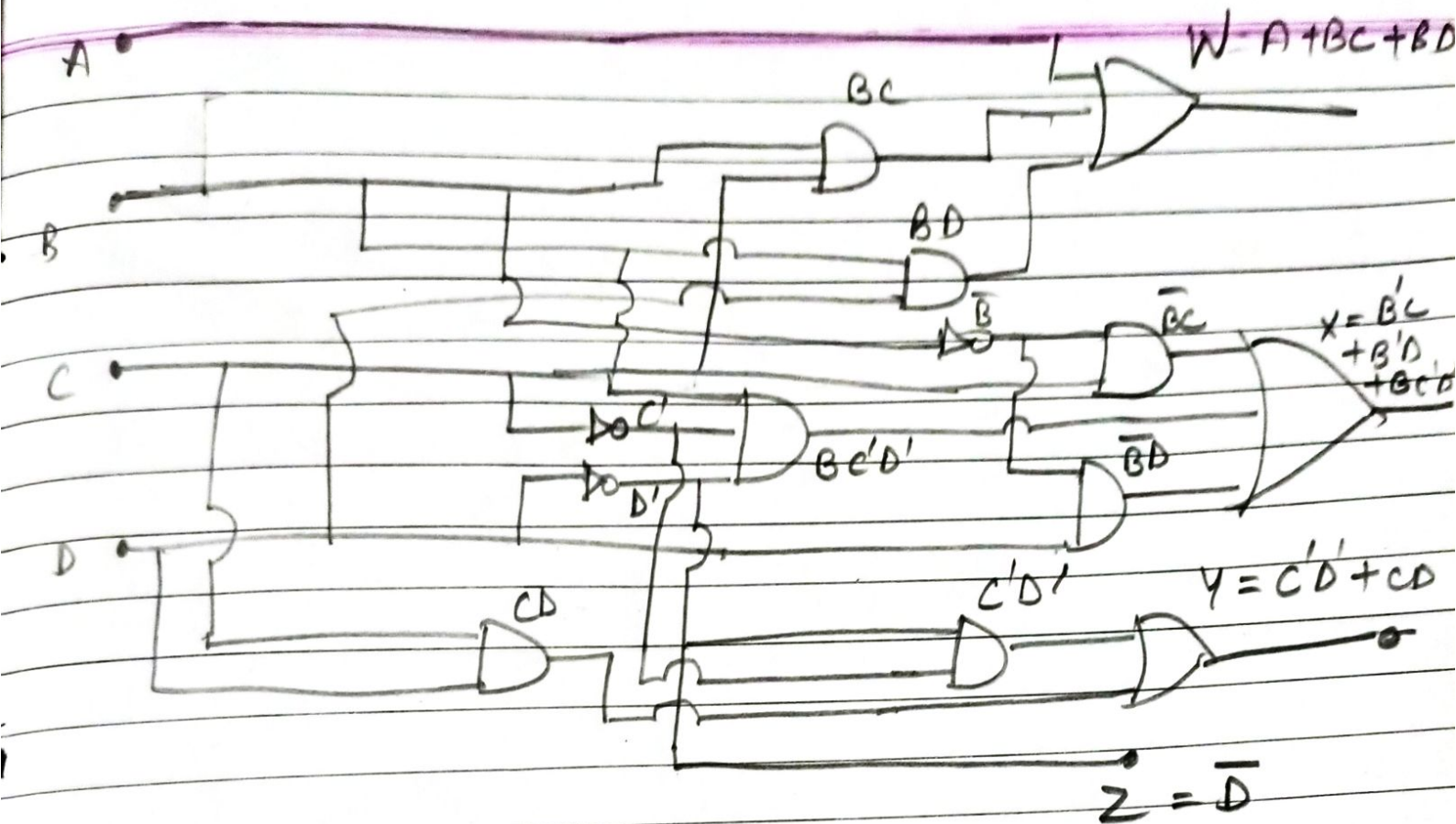

Egs :- $(100001011001)_{BCD} \rightarrow (\quad)_{\text{excess 3}}$

Step I $\rightarrow$ Make a group of 4-bit

Step II
 $\rightarrow$ Add 0011
 to each 4-bit group

1000	0101	1001
0011	0011	0011
<u>1011</u>	<u>1000</u>	<u>1100</u>

Ans $\rightarrow (101110001100)_{\text{excess 3}}$